

CS 222 Lec 11

from last time

$$\text{circuit fn} = (a + b \cdot c) \cdot (a' \cdot b)'$$

$$= \underline{(a + bc)} \cdot (a + b')$$

$$= (a + bc) \cdot a + (a + bc) \cdot b'$$

$$= a + ab' + bcb'$$

$$= a + ab' + 0$$

$$= a + ab'$$


$$= a$$

"absorption"

$$a \cdot (a + b) = a$$

$$a + a \cdot b = a$$

(dual)

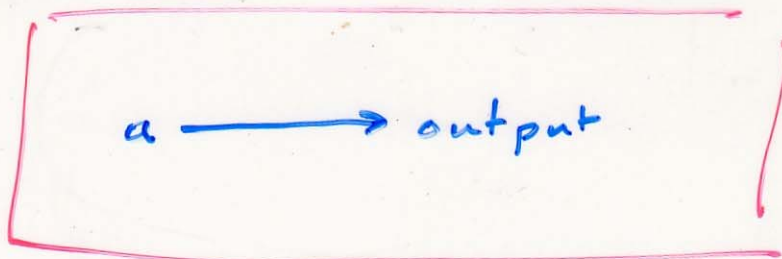

minimal circuit
(0 gates)

Boolean Functions


a	b	c	f
0	0	0	1
0	0	1	0
			↓
	⋮		⋮
1	1	1	

there are
 $2^8 = 256$
possible
boolean fns
on 3
inputs.

must
specify
this column

n inputs

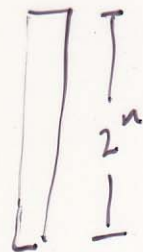⇒ must specify a
binary column of
length 2^n



⇒ there are
 2^{2^n} such strings

inputs			output
a	b	c	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

'ON-set'

Sum of Products Representation

$$f(a,b,c) = a'b'c + a'bc + ab'c' + abc'$$

⇓
Karnaugh Maps
Simplified
S.O.P

Karnaugh Maps

$$f(x, y) = xy' + x'y'$$

$$= (x + x') \cdot y'$$

$$= 1 \cdot y'$$

$$= y'$$

	y	y'
x	0	1
x'	0	1

simplified $f = y'$

$f(x, y)$

	y	y'
x	1	1
x'	1	0

simplified $f = x + y$


full S-o-P = $xy + x'y + xy'$

K-Maps for 3 variables

	yz	yz'	$y'z'$	$y'z$
x	0	1	1	0
x'	1	0	0	1

$$f(x, y, z) = x'y'z + x'yz + xy'z' + xyz'$$

$$\text{simplified } f = xz' + x'z$$

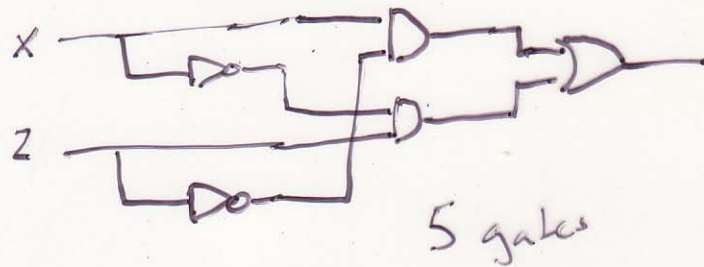

with XOR-gate \rightarrow 1 gate

f

	yz	yz'	$y'z'$	$y'z$
x	1	1	0	0
x'	1	1	1	1

$$f = x' + y$$

4 variable case $\{w, x, y, z\}$

	zw	zw'	$z'w'$	$z'w$
xy	0	0	0	0
xy'	1	1	1	1
$x'y'$	1	1	1	1
$x'y$	0	1	1	0