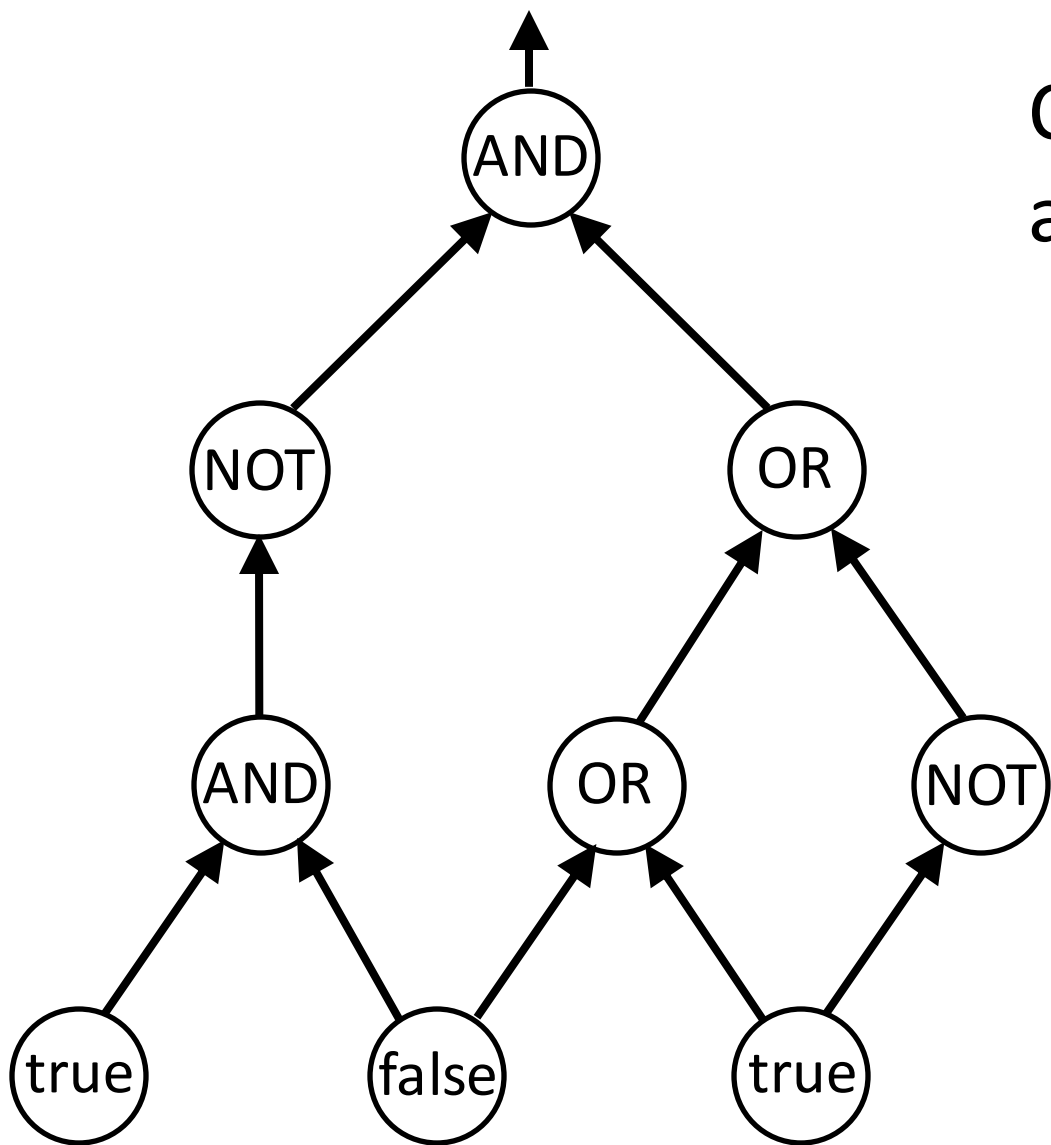



Linear Programming

CSCI 432




Circuit Value Problem: When the gates are evaluated, is the output true?

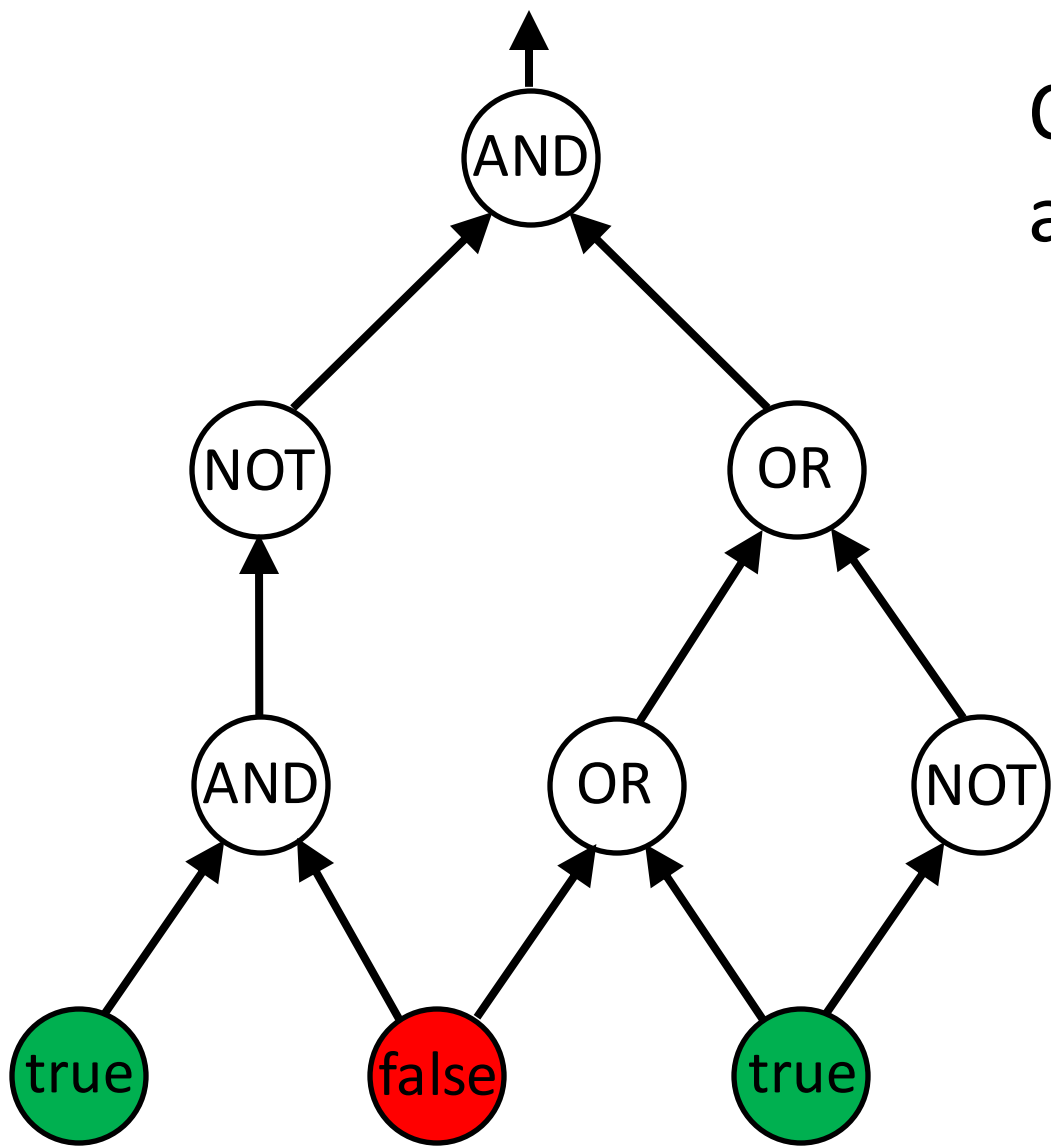Given a circuit schematic, what is the answer?




Circuit Value Problem: When the gates are evaluated, is the output true?

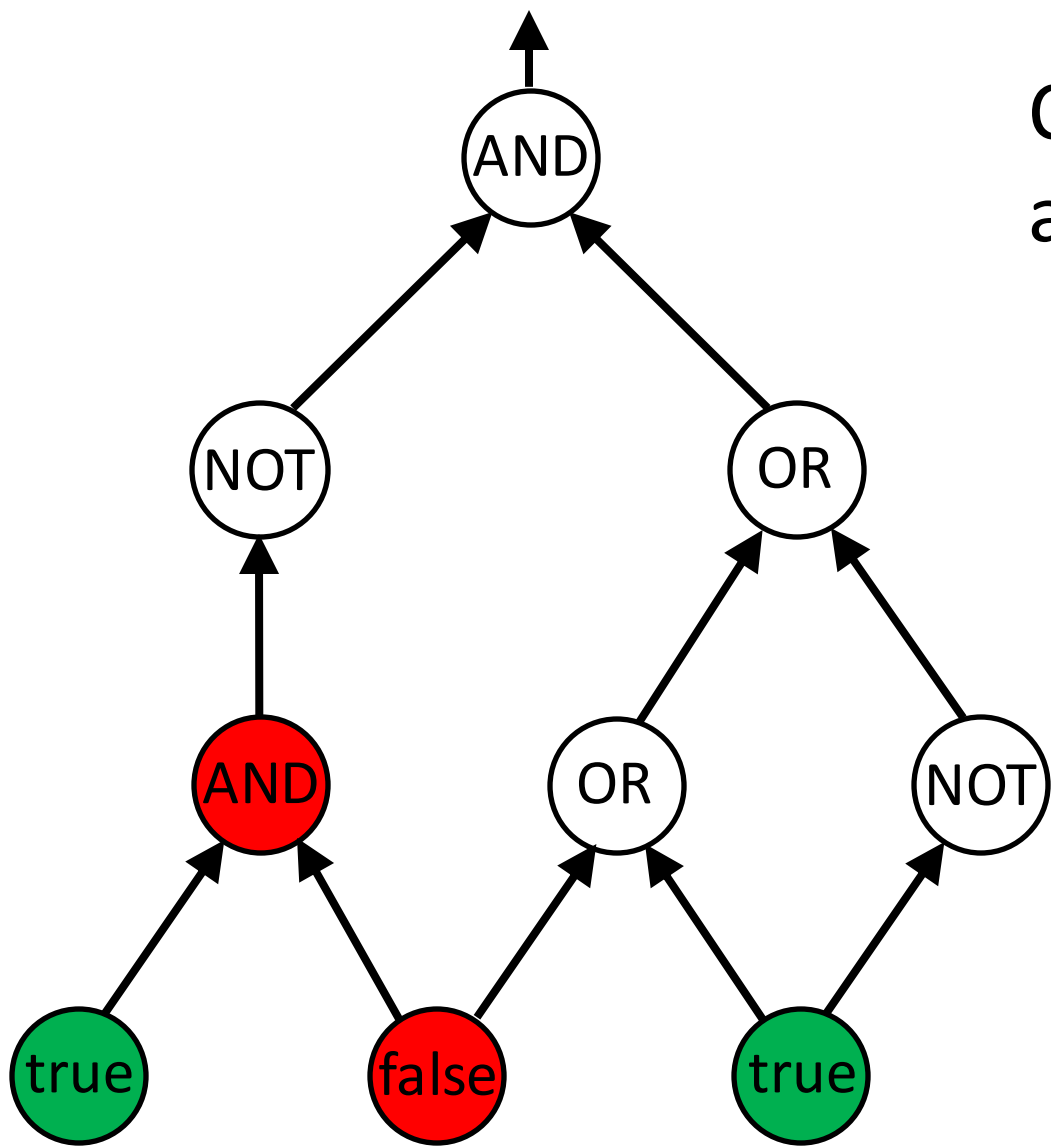Given a circuit schematic, what is the answer?




Circuit Value Problem: When the gates are evaluated, is the output true?

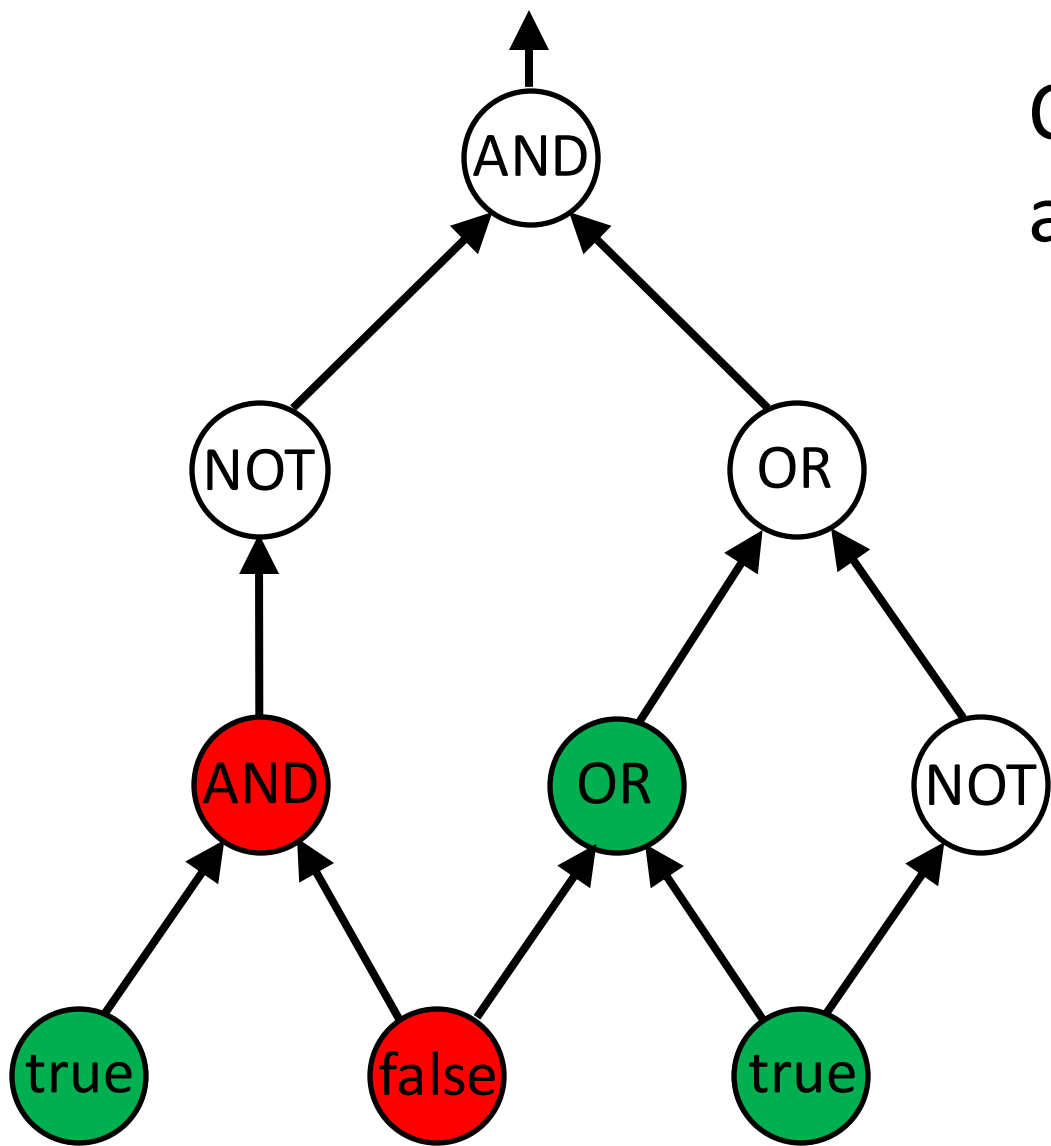Given a circuit schematic, what is the answer?




Circuit Value Problem: When the gates are evaluated, is the output true?

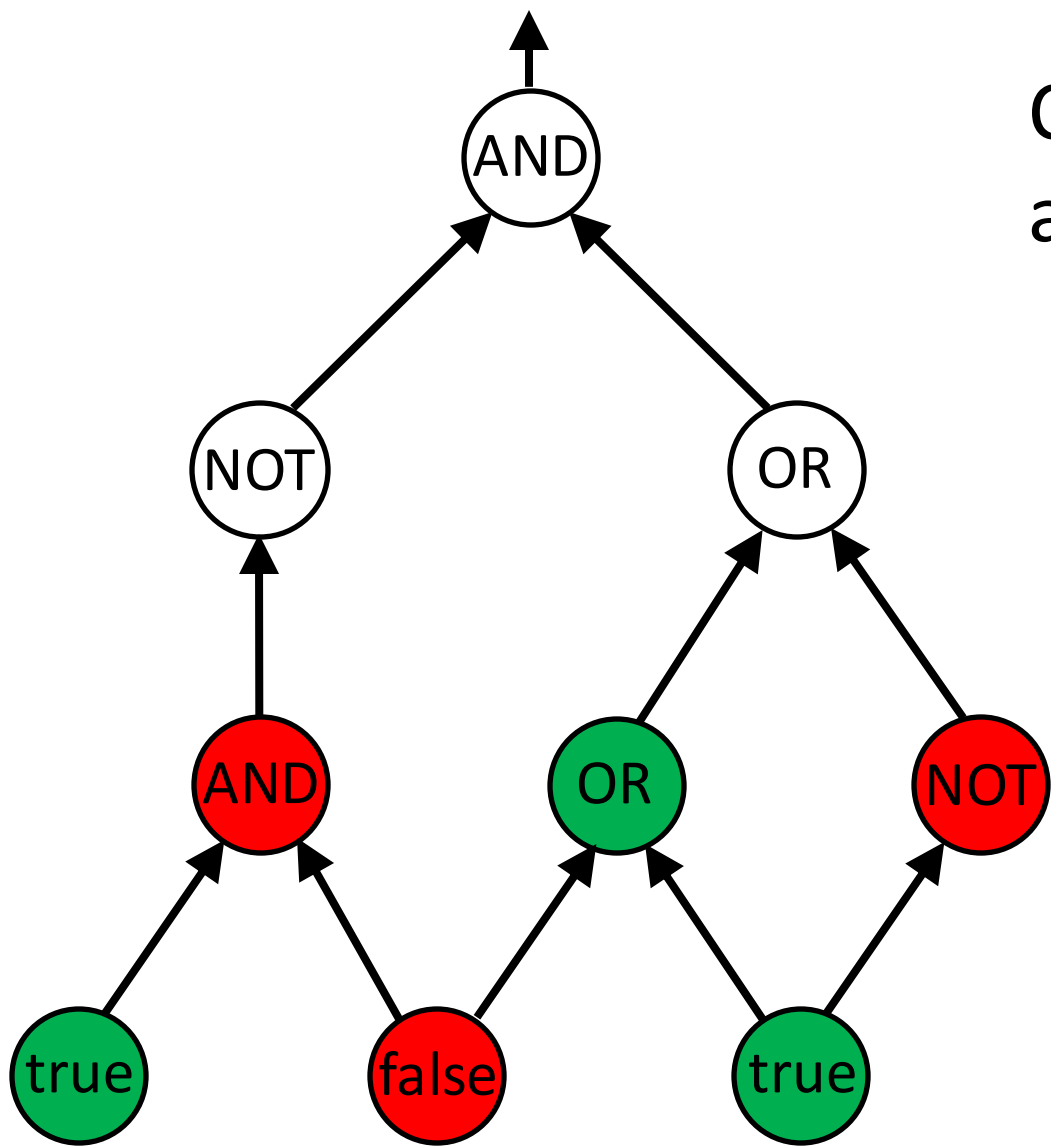Given a circuit schematic, what is the answer?




Circuit Value Problem: When the gates are evaluated, is the output true?

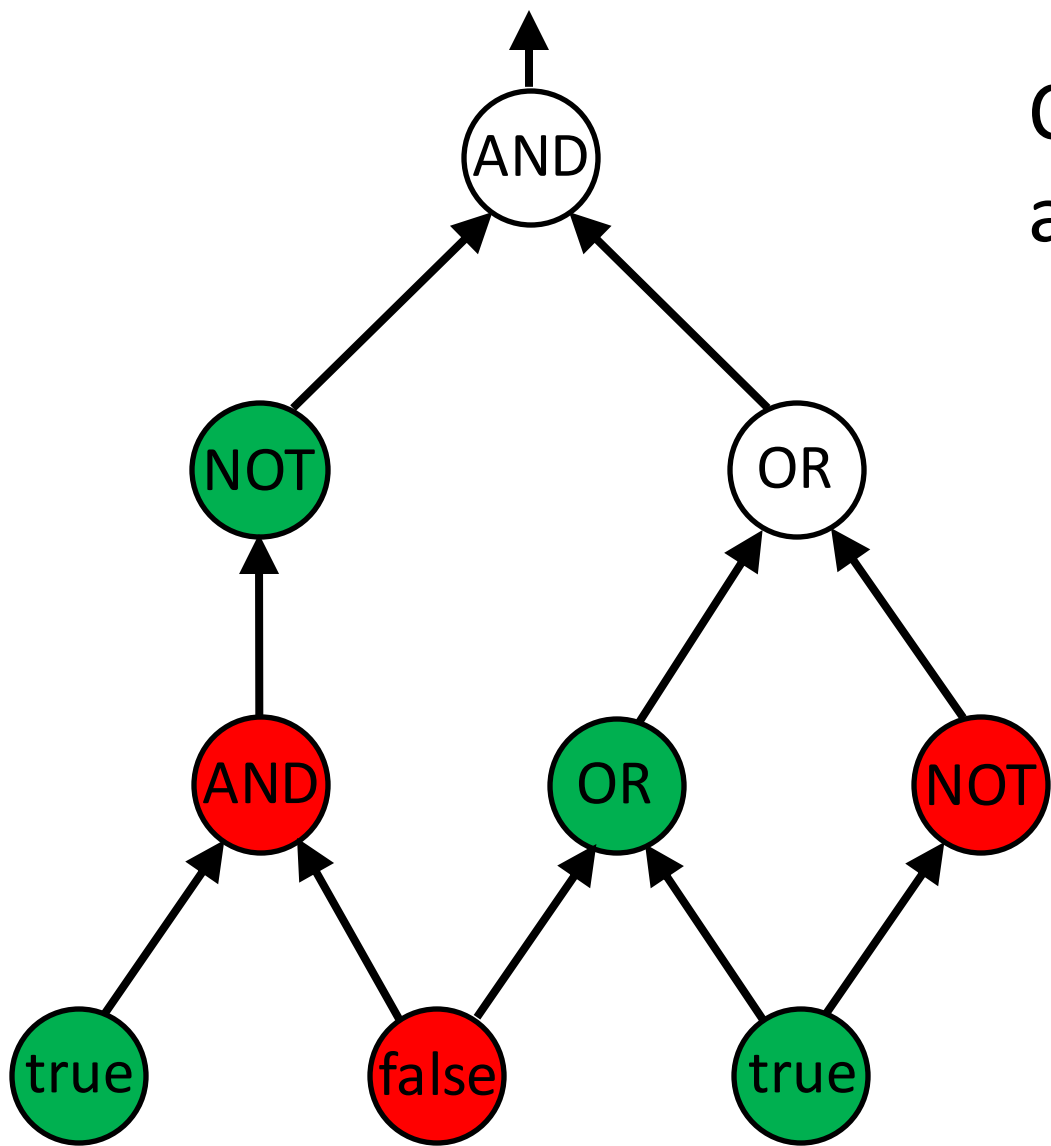Given a circuit schematic, what is the answer?




Circuit Value Problem: When the gates are evaluated, is the output true?

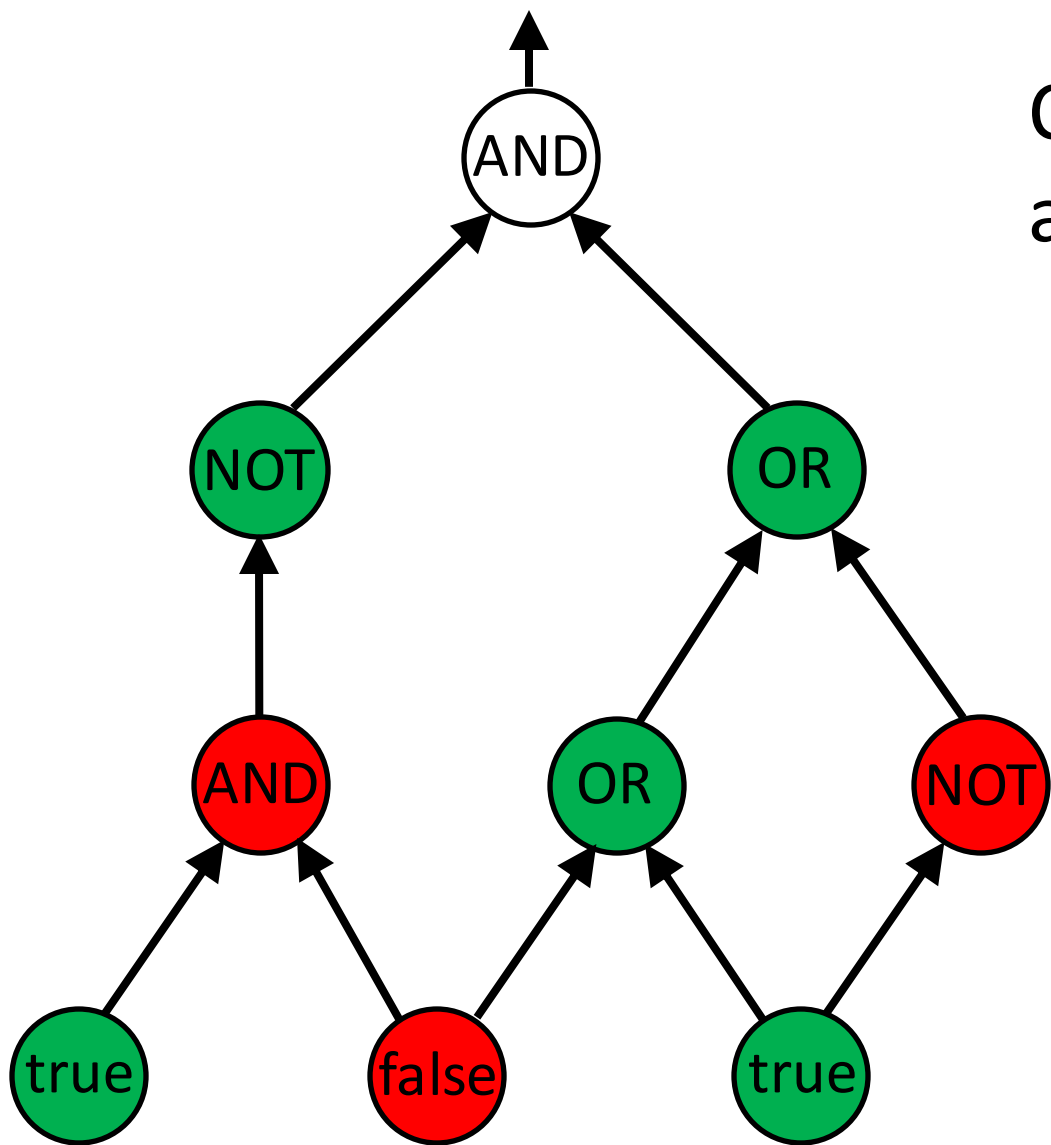Given a circuit schematic, what is the answer?




Circuit Value Problem: When the gates are evaluated, is the output true?

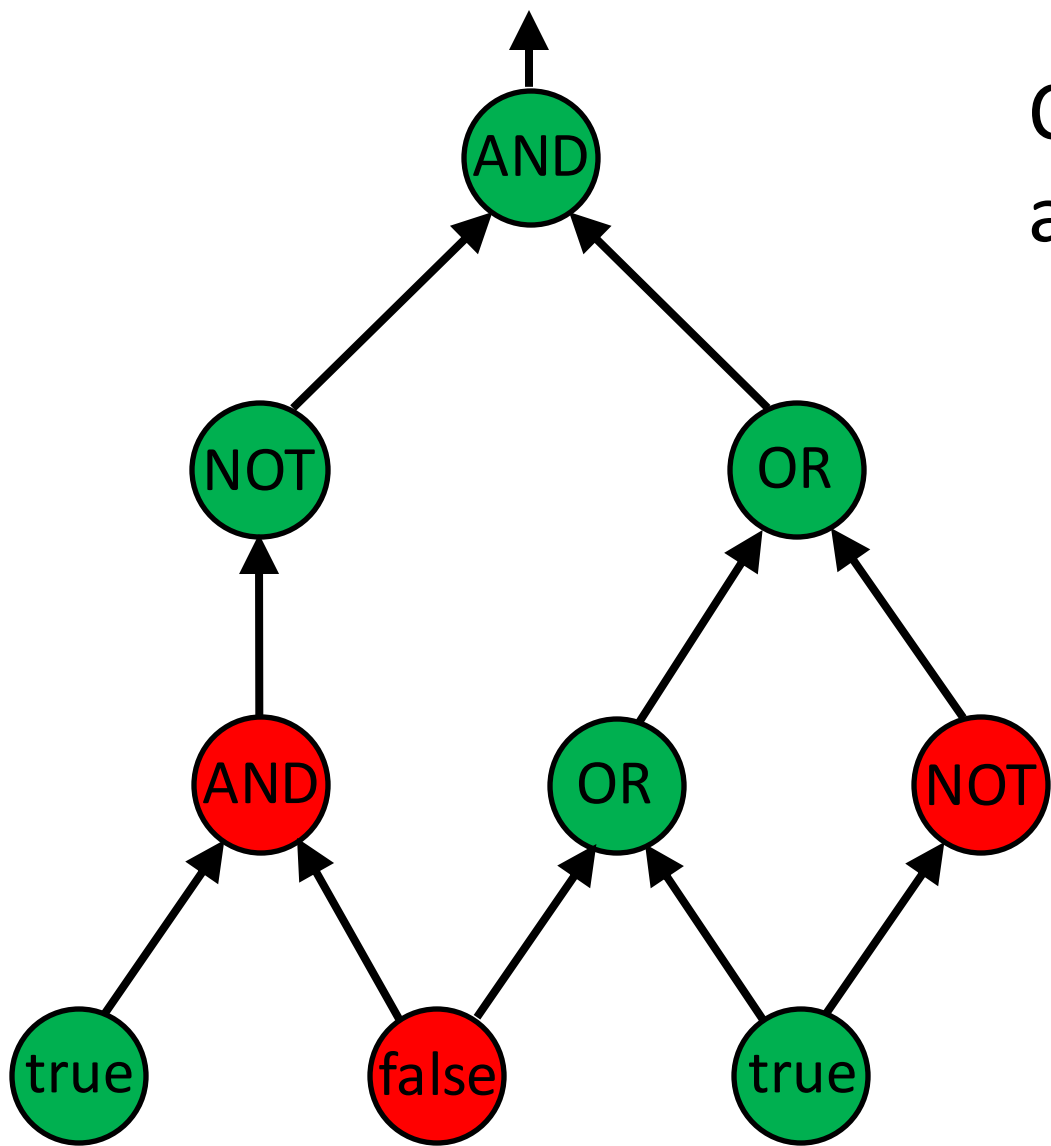Given a circuit schematic, what is the answer?



Circuit Value Problem: When the gates are evaluated, is the output true?

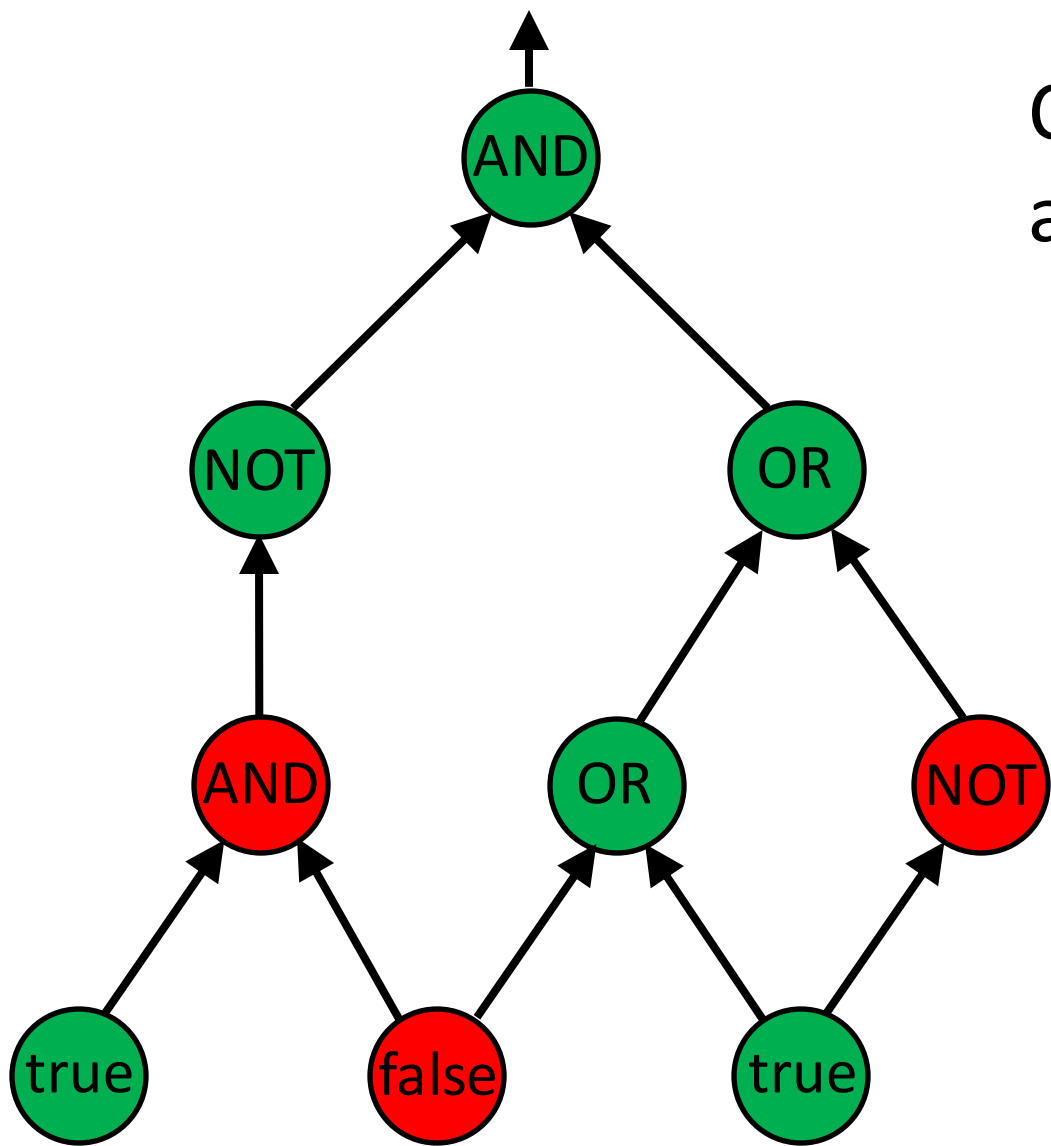Given a circuit schematic, what is the answer?



Circuit Value Problem: When the gates are evaluated, is the output true?


Given a circuit schematic, what is the answer?

Can we make a Linear Program that solves this?




Circuit Value Problem: When the gates are evaluated, is the output true?

x_i = gate's evaluated value

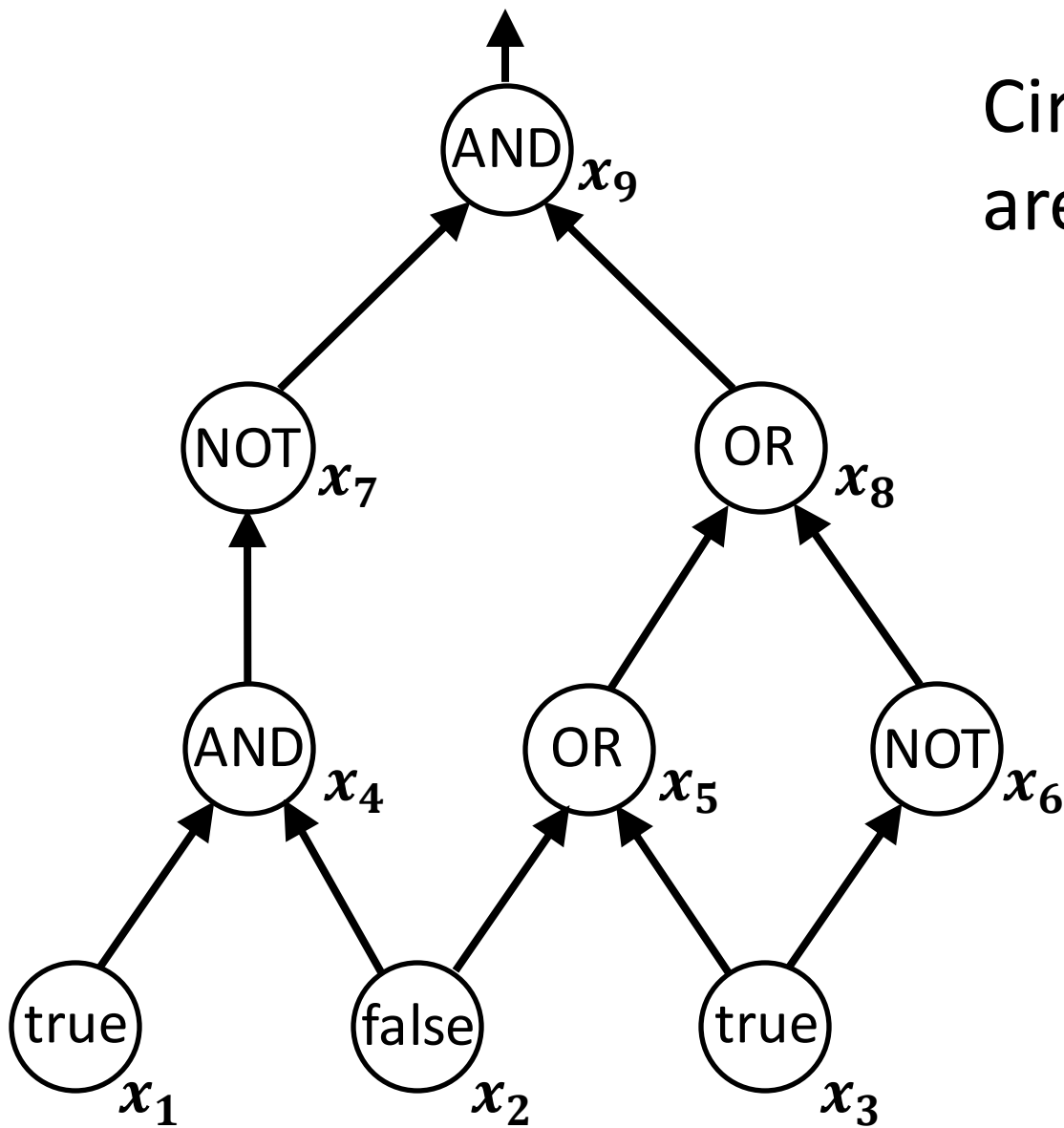


Circuit Value Problem: When the gates are evaluated, is the output true?

x_i = gate's evaluated value

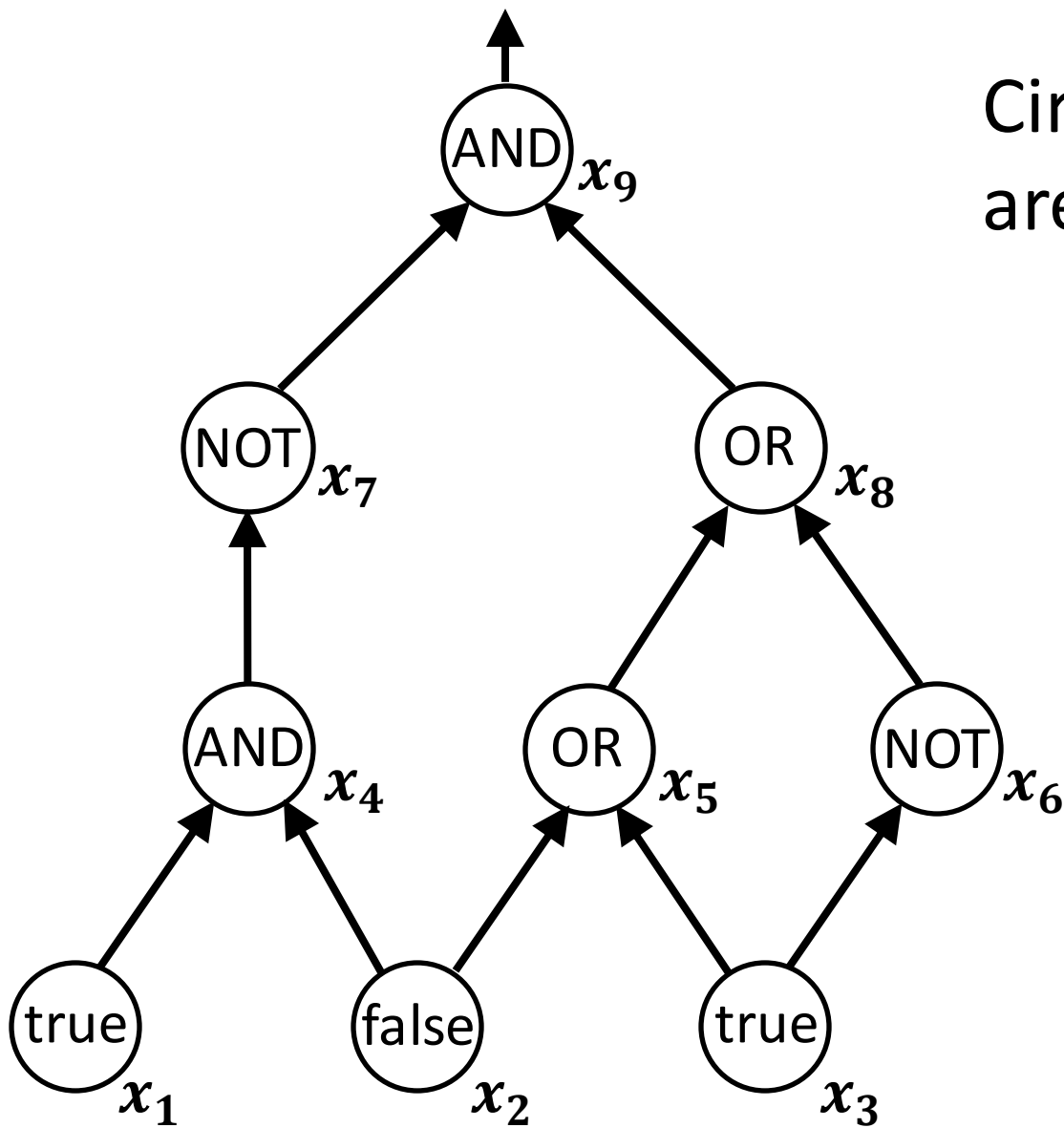

What is x_9 's value?

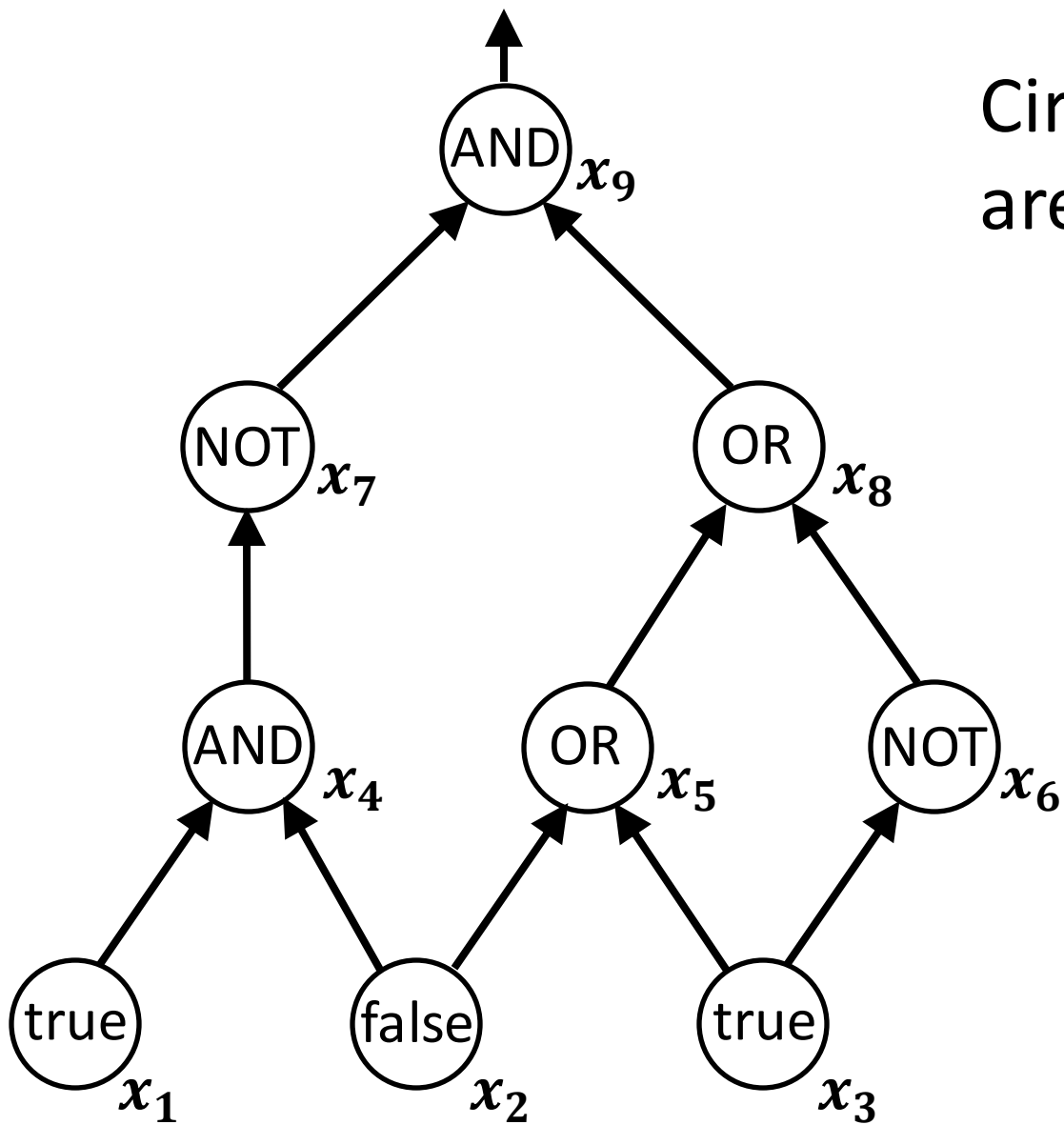
Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

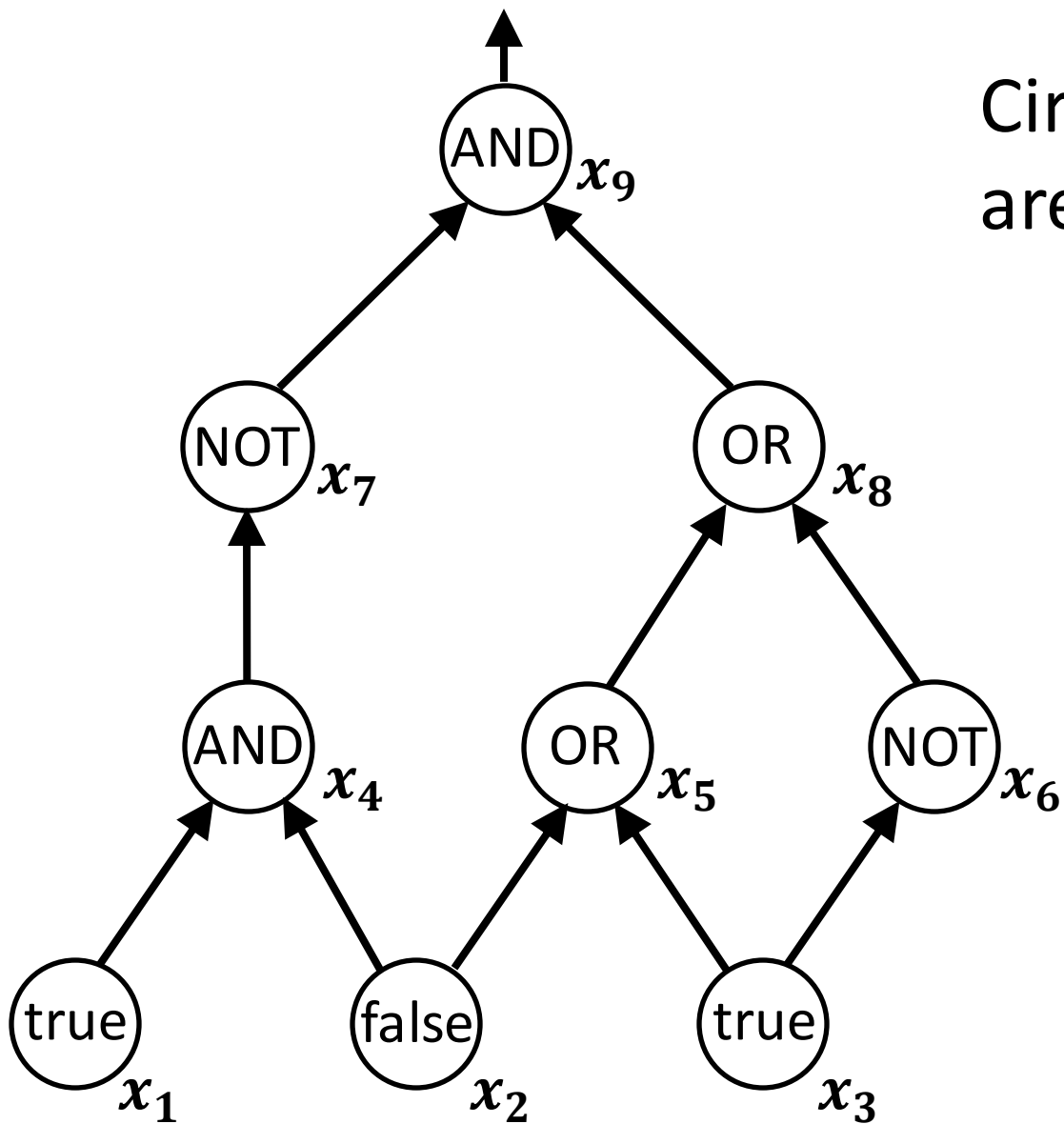Circuit Value Problem: When the gates are evaluated, is the output true?




x_i = gate's evaluated value

Objective: ??

Subject to:

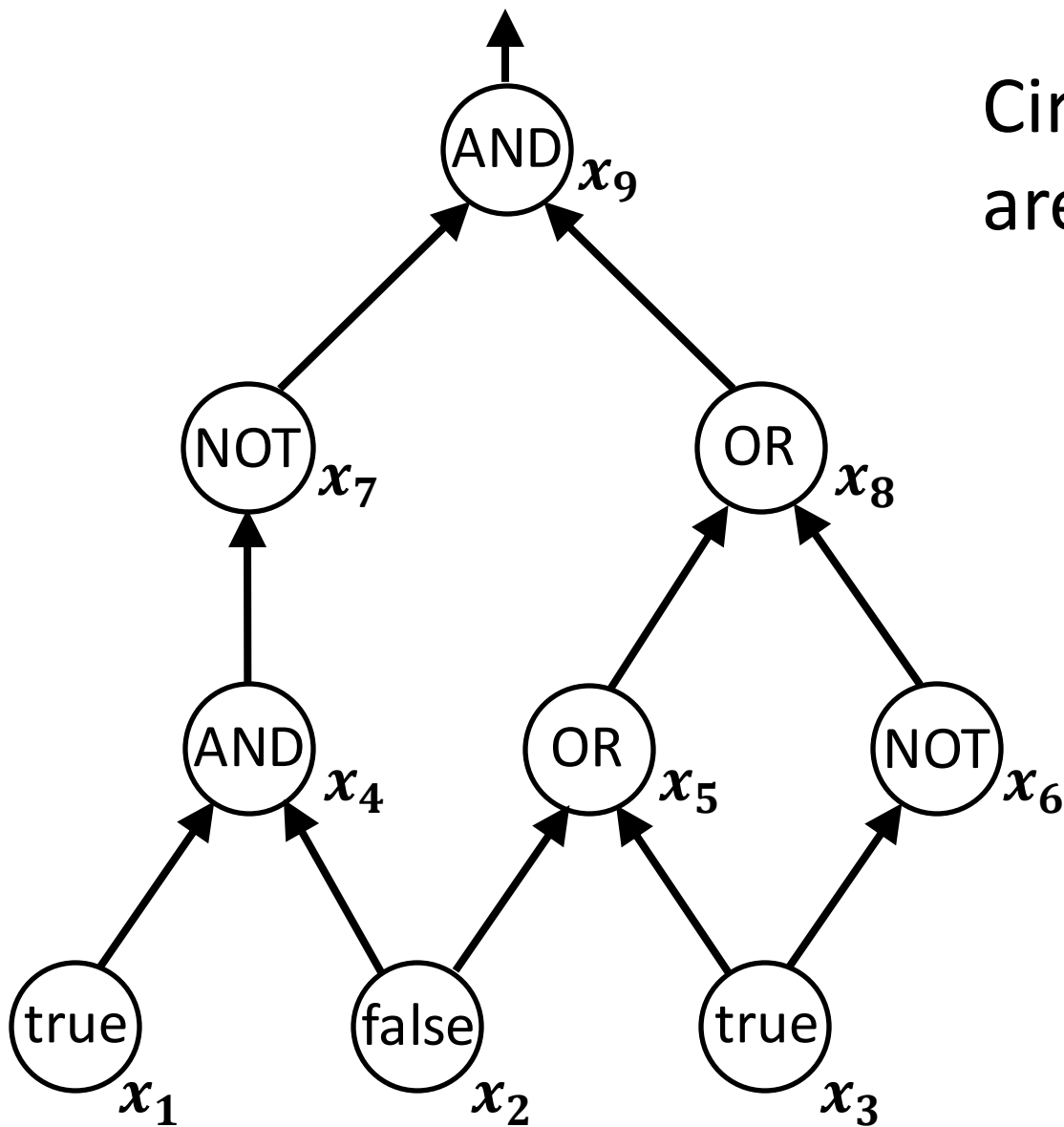
Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in \{0,1\}, \forall i$

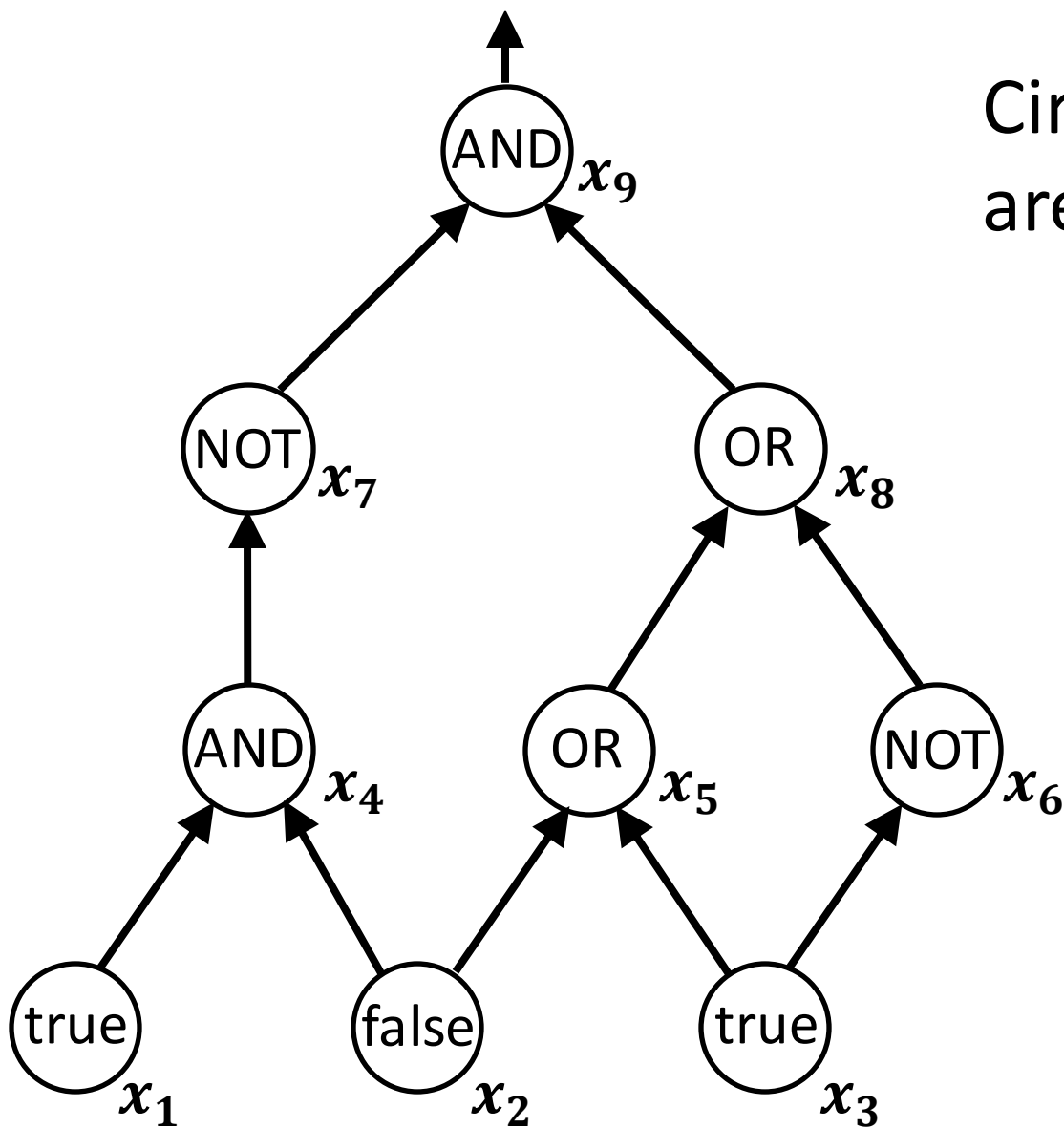

Circuit Value Problem: When the gates are evaluated, is the output true?


x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

We need $x_i \in \{0, 1\}$, but maybe we can make that happen without forcing it to be an ILP.

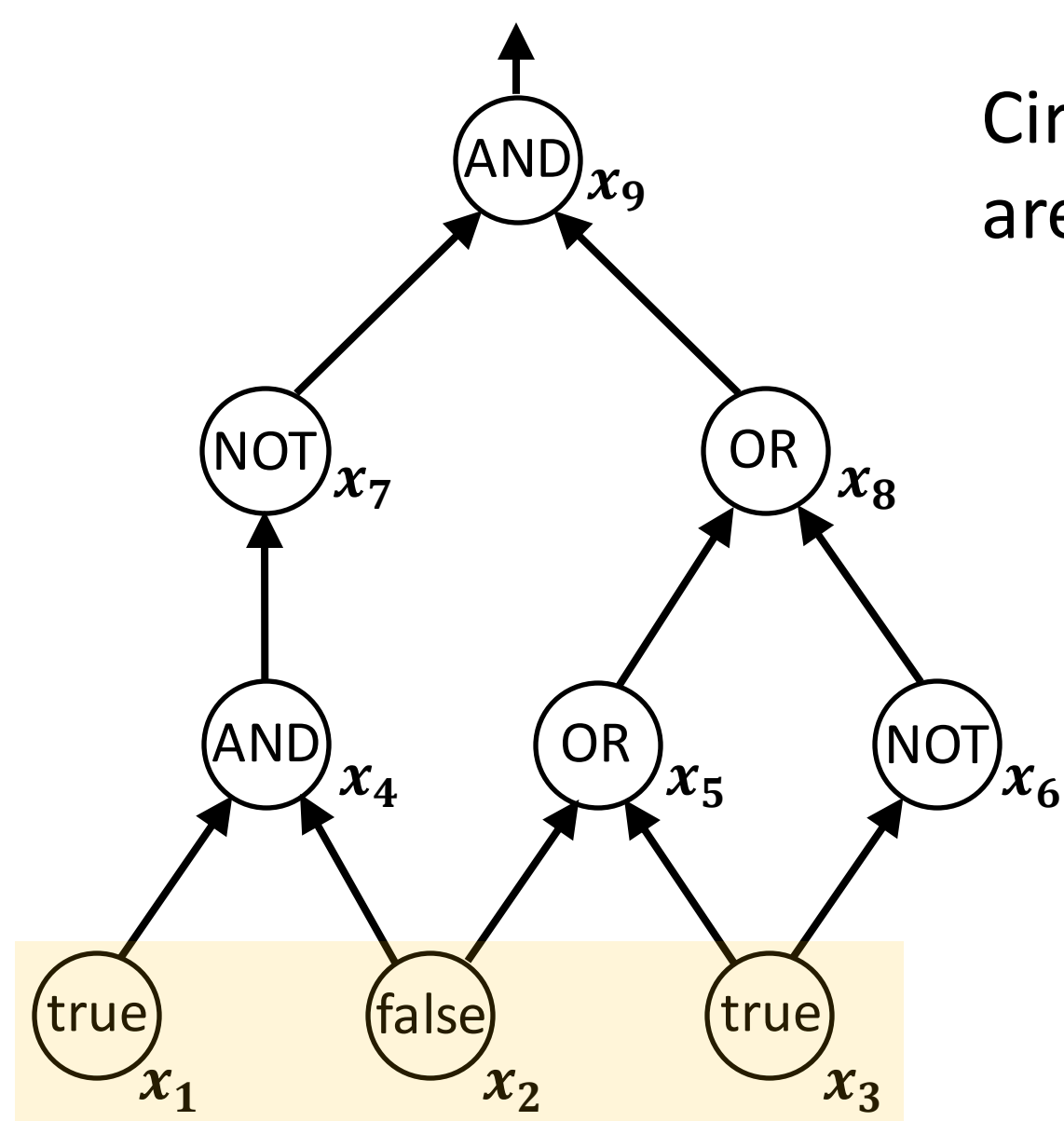Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$x_1 = ?$

$x_2 = ?$

$x_3 = ?$

Circuit Value Problem: When the gates are evaluated, is the output true?

x_i = gate's evaluated value

Objective: ??


Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$


$$x_2 = 0$$

$$x_3 = 1$$

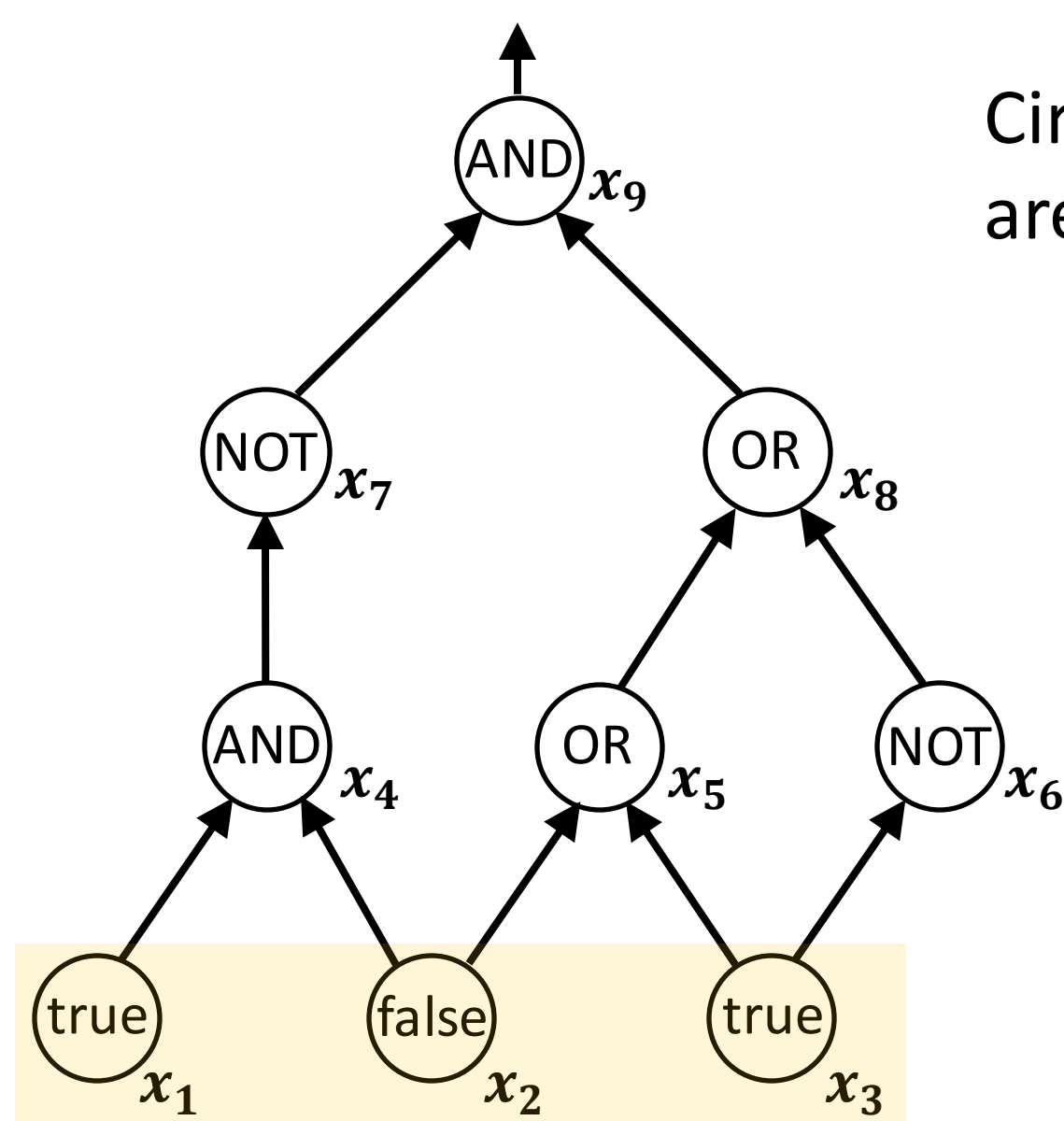In general, if gate i is initialized to true (or false), make $x_i = 1$ (or 0).



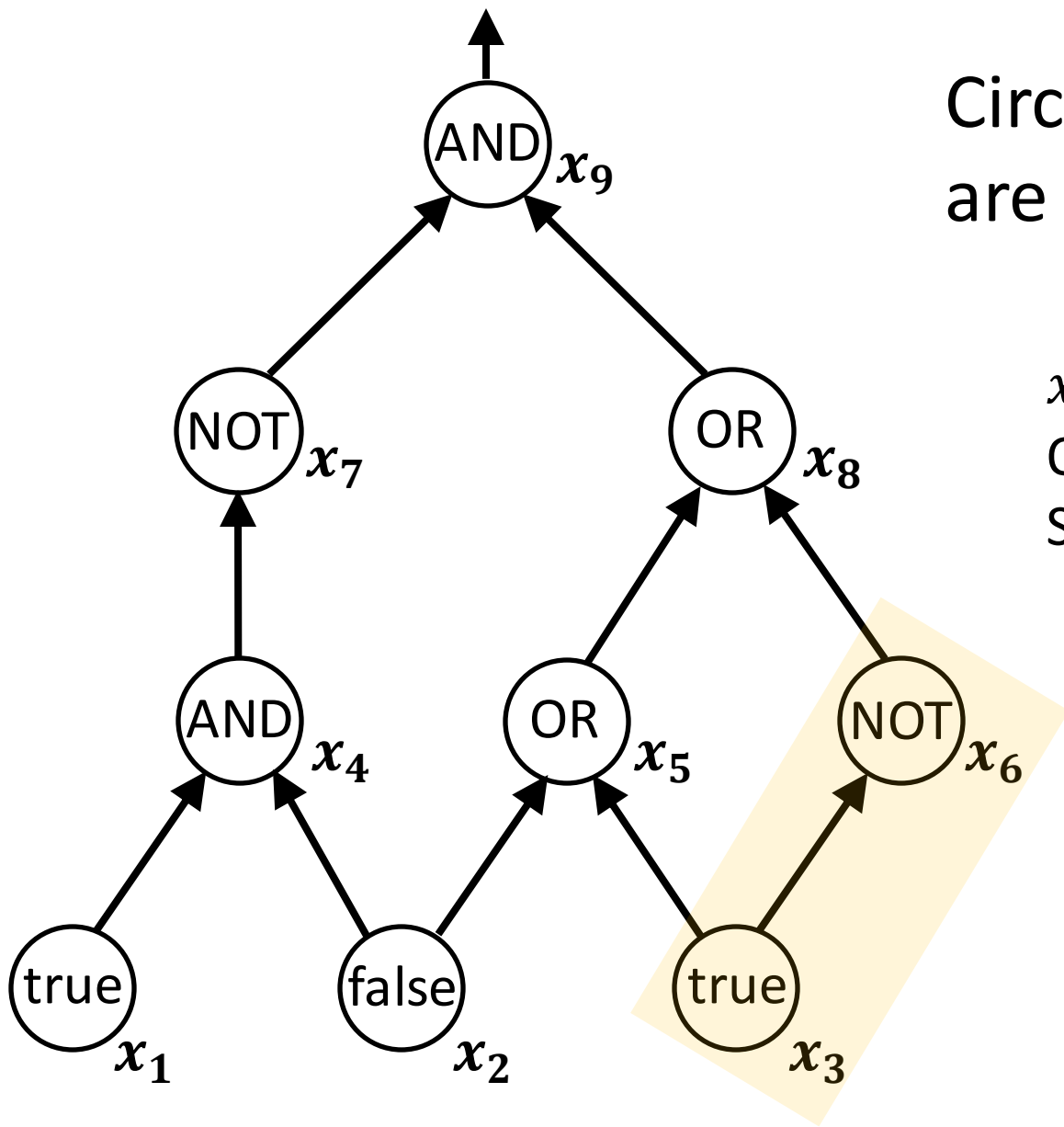Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$


$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = ??$$

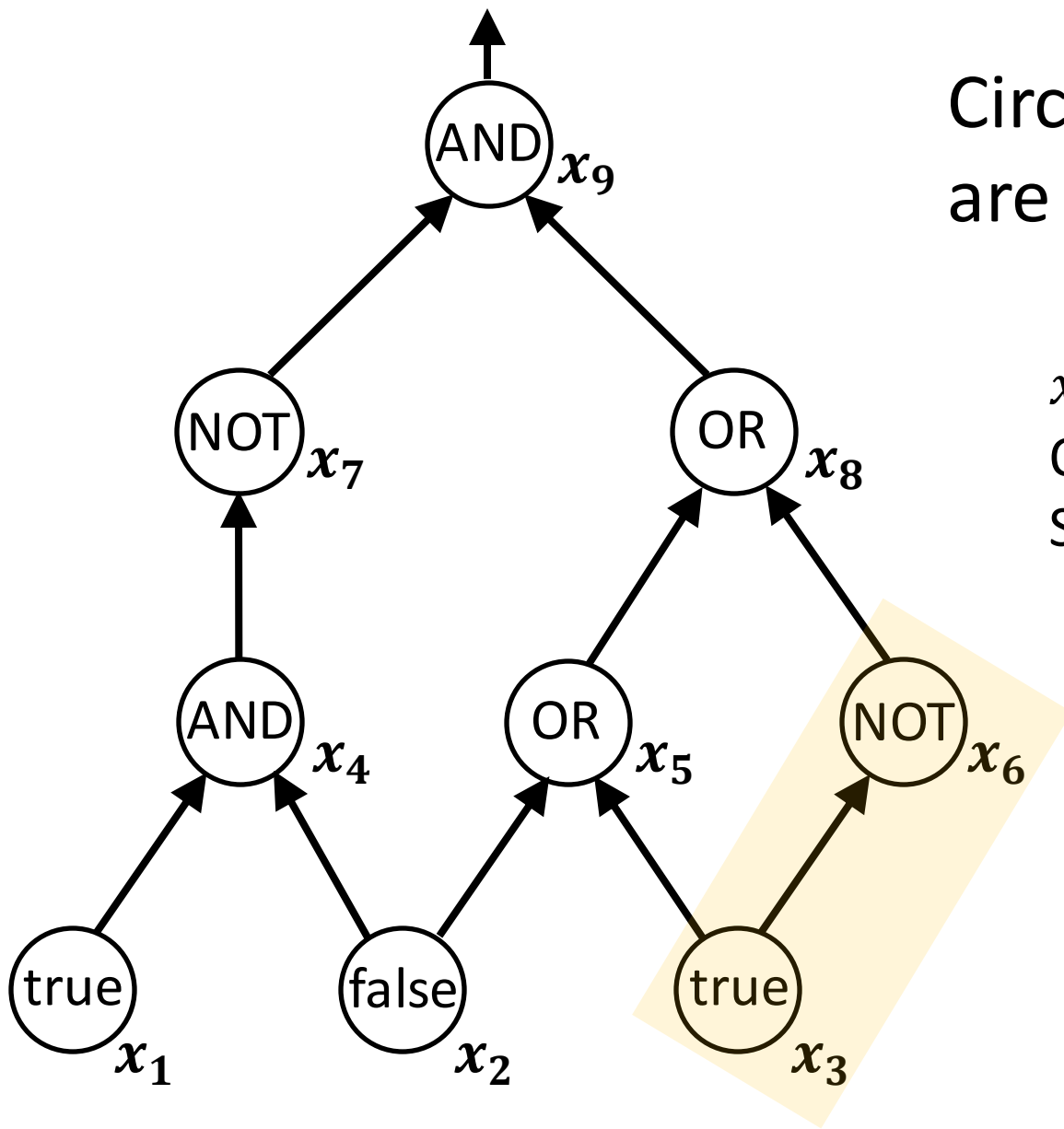Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$


$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

In general, if gate i is NOT gate j , make $x_i = 1 - x_j$

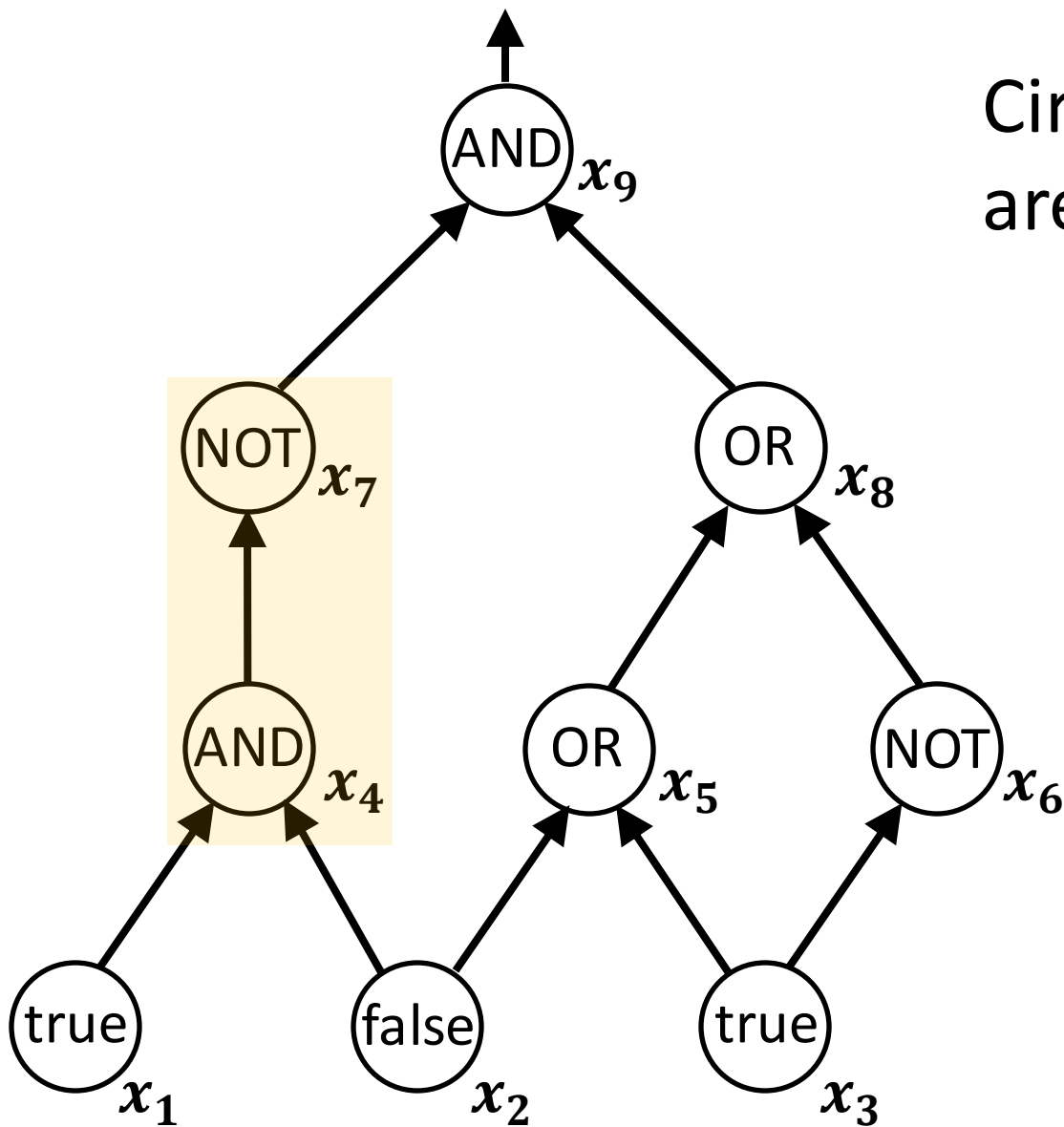Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$


$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

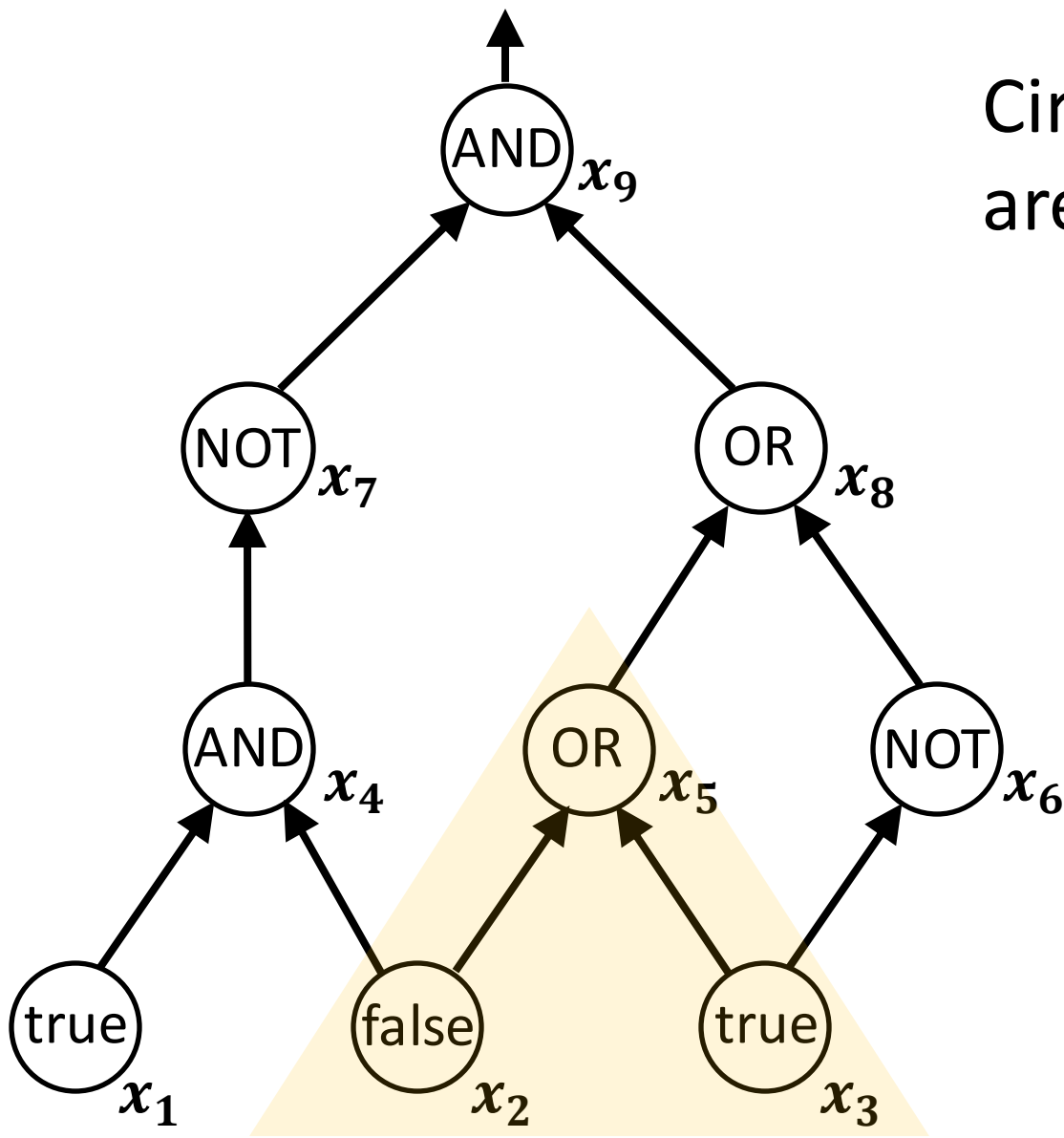Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$


$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

??

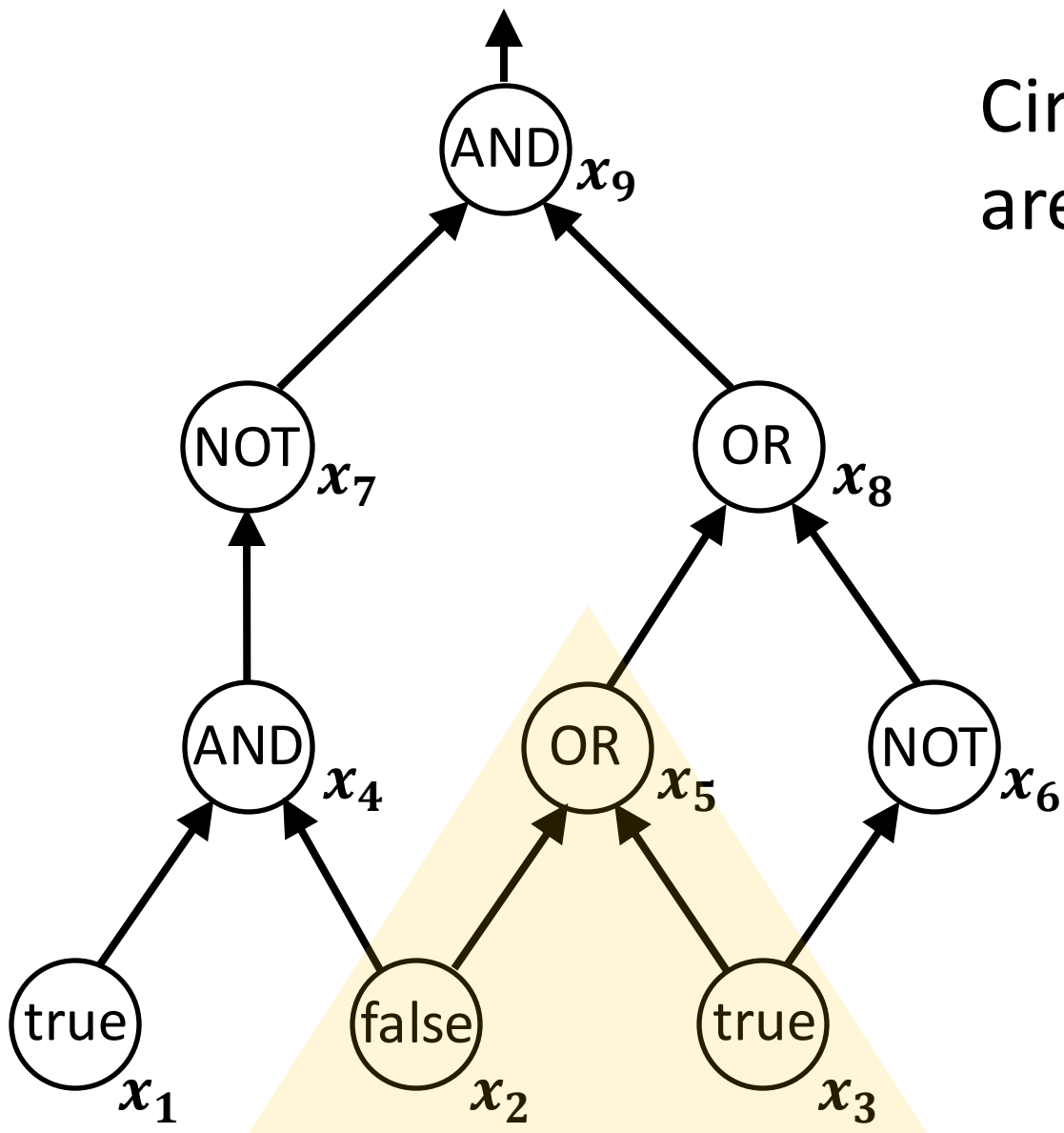Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$


$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

x_j	x_k	$x_i = x_j \text{ OR } x_k$
0	0	0
1	0	1
0	1	1
1	1	1

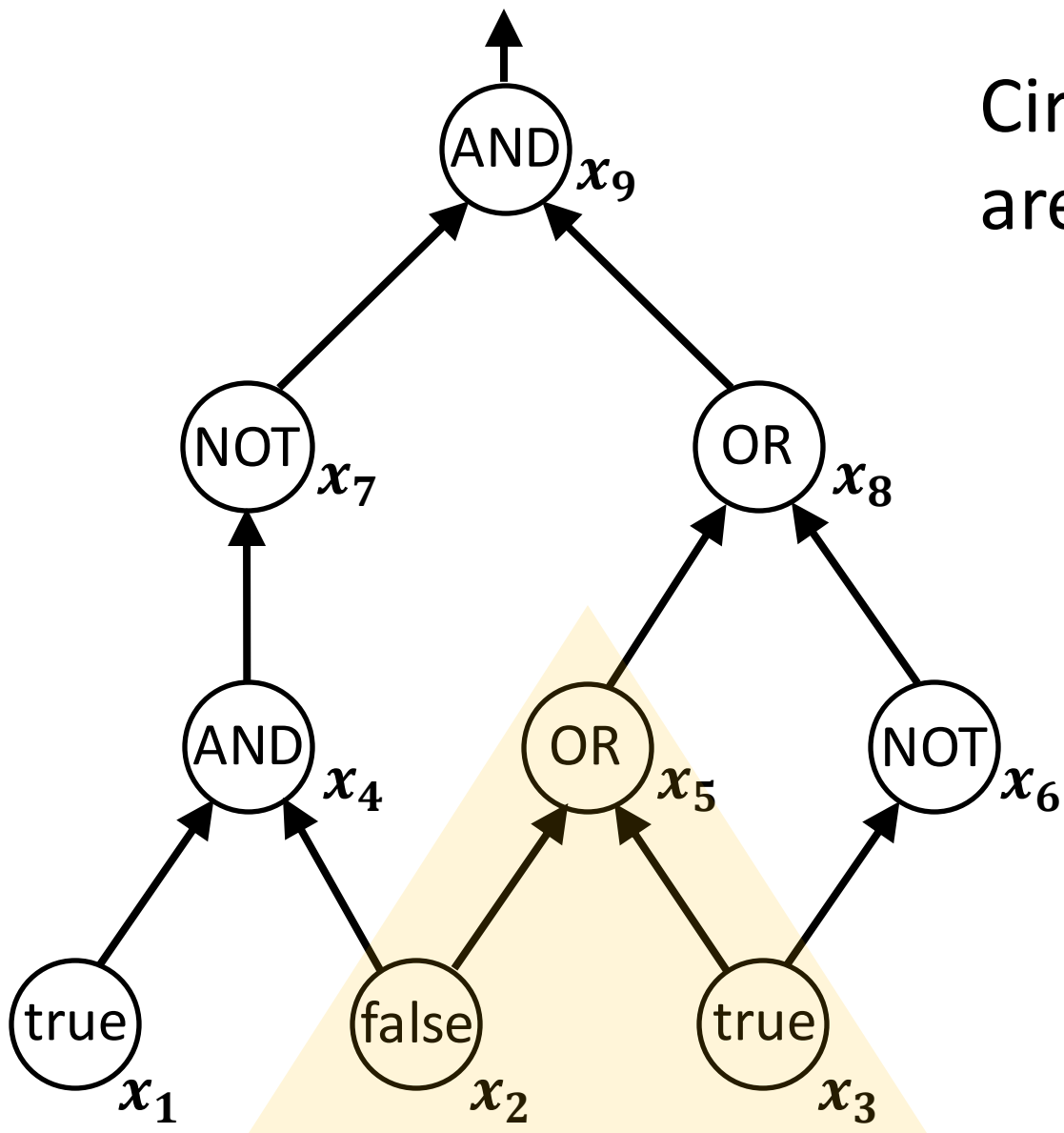Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$


$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

x_j	x_k	$x_i = x_j \text{ OR } x_k$
0	0	0
1	0	1
0	1	1
1	1	1

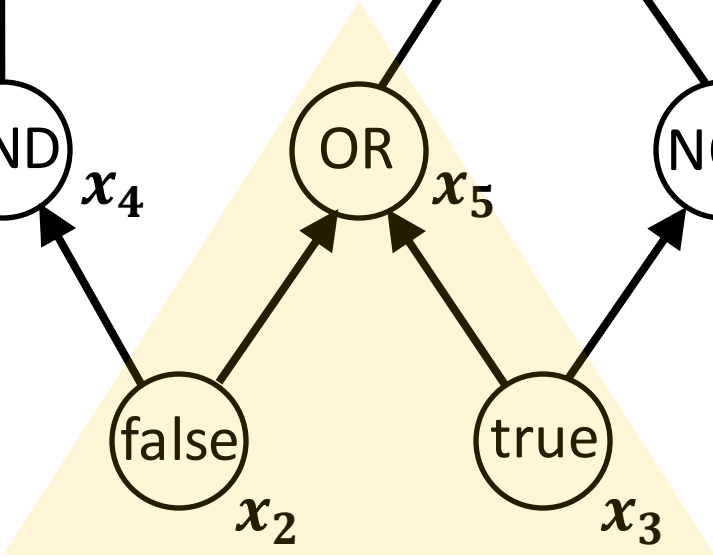
$$x_i = \text{gate's evaluated value}$$

Subject to: $x_i \in [0,1], \forall i$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$


$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

x_j	x_k	$x_i = x_j \text{ OR } x_k$
0	0	0
1	0	1
0	1	1
1	1	1

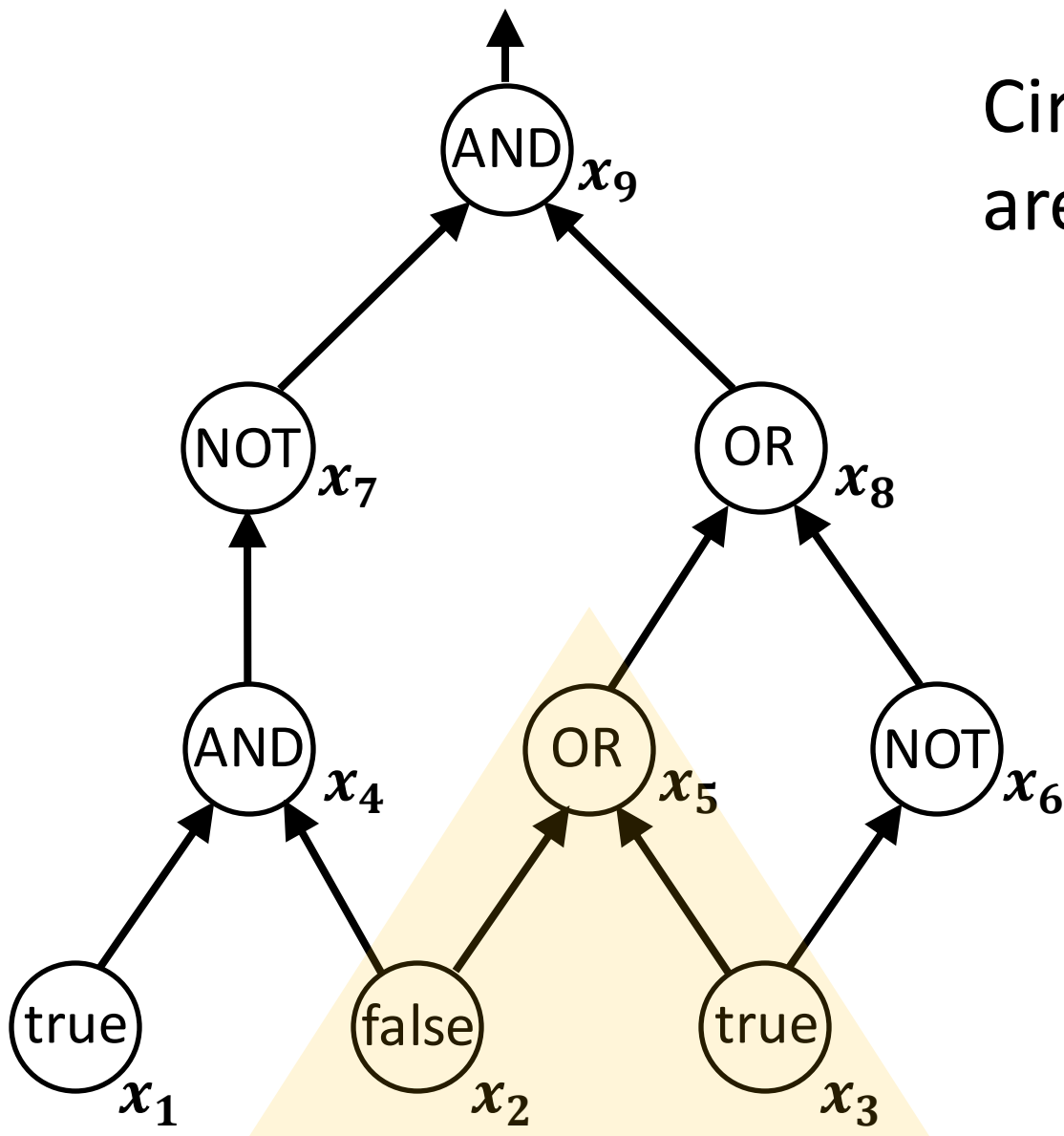Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$


$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

x_j	x_k	$x_i = x_j \text{ OR } x_k$
0	0	0
1	0	1
0	1	1
1	1	1

Is that enough?

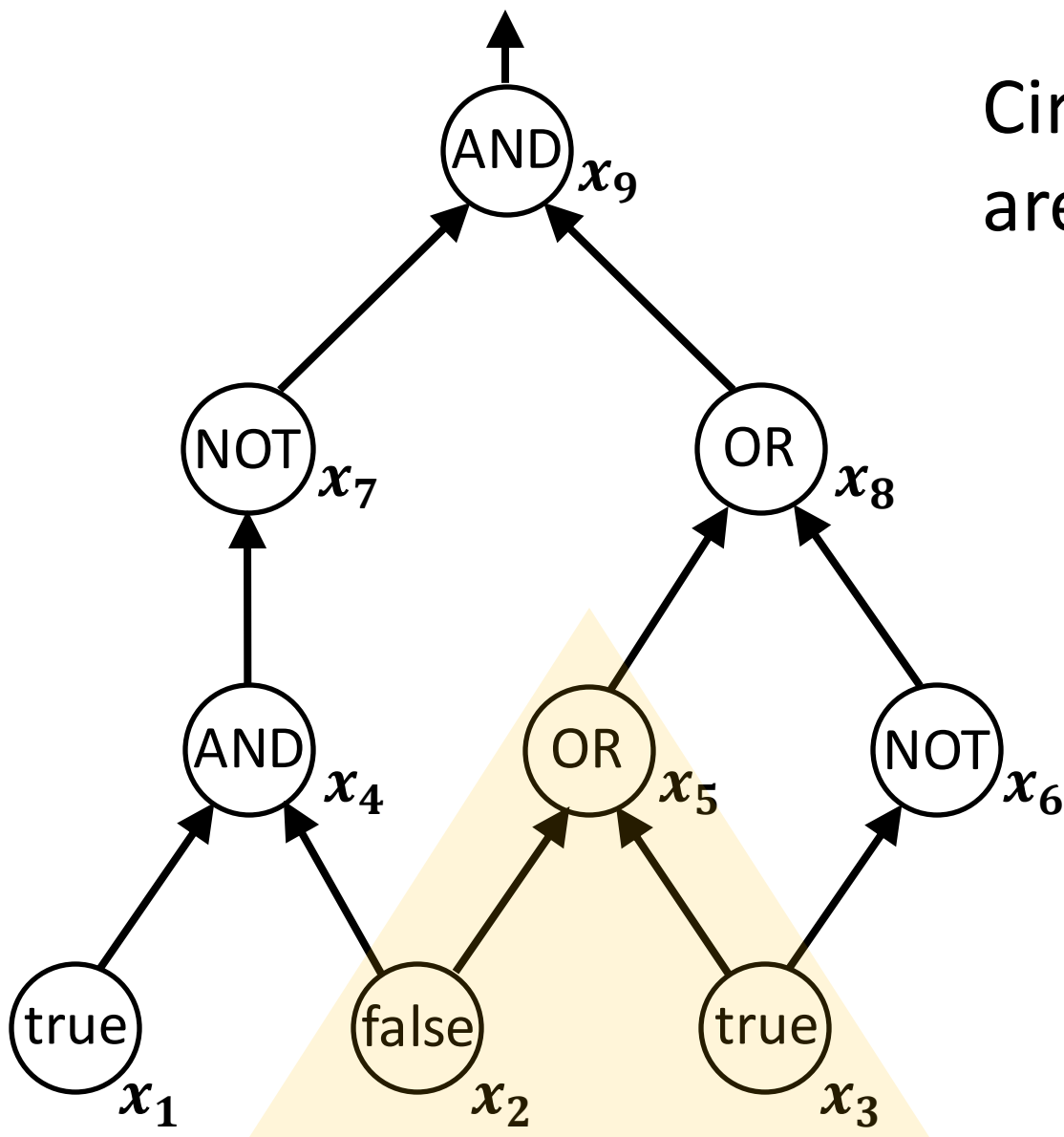Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$


$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

$$x_5 \leq x_2 + x_3$$

x_j	x_k	$x_i = x_j \text{ OR } x_k$
0	0	0
1	0	1
0	1	1
1	1	1

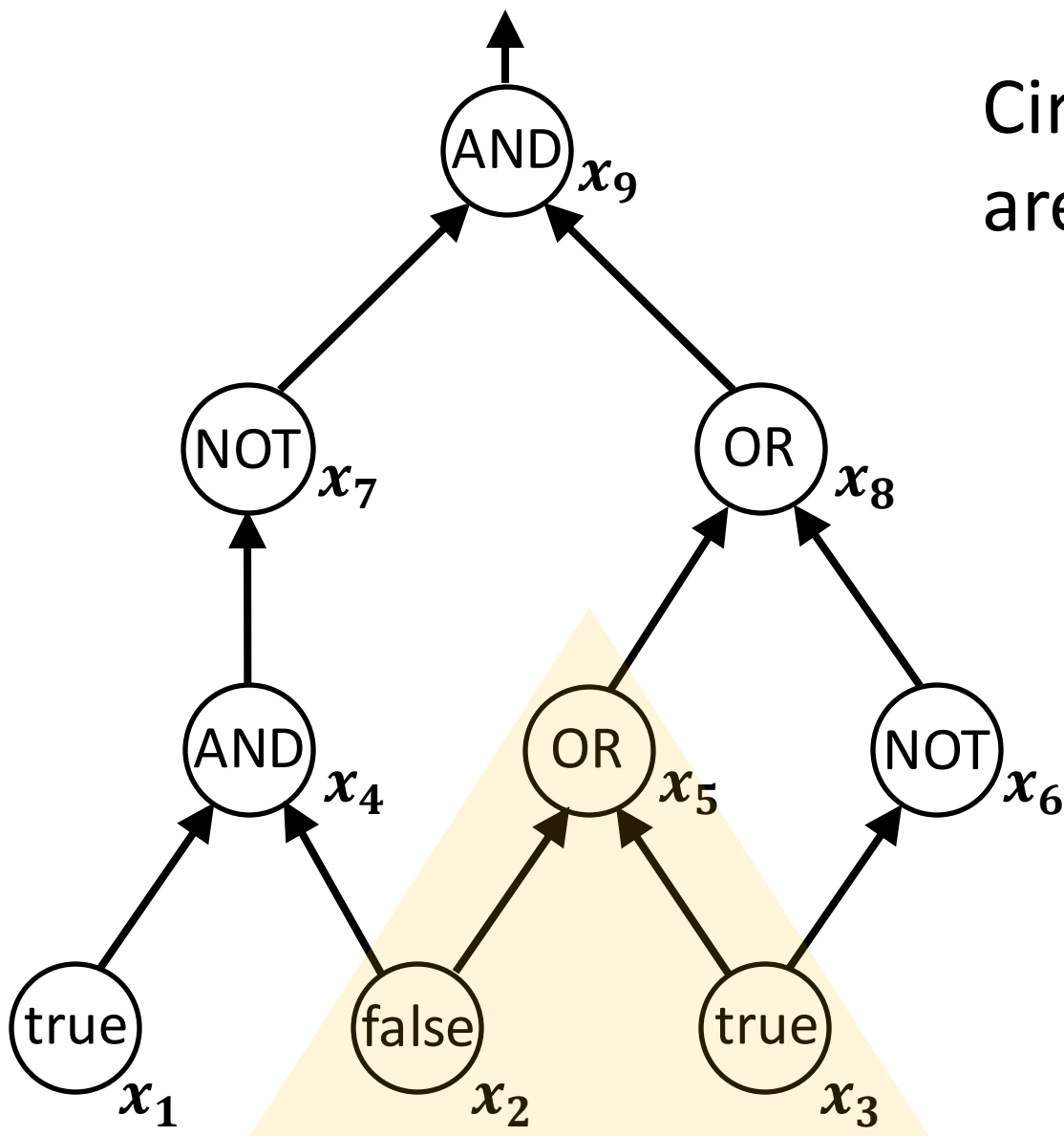

Circuit Value Problem: When the gates are evaluated, is the output true?

x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

$$x_5 \leq x_2 + x_3$$


In general, if gate i is OR gates j, k :

$$x_i \geq x_j$$

$$x_i \geq x_k$$

$$x_i \leq x_j + x_k$$

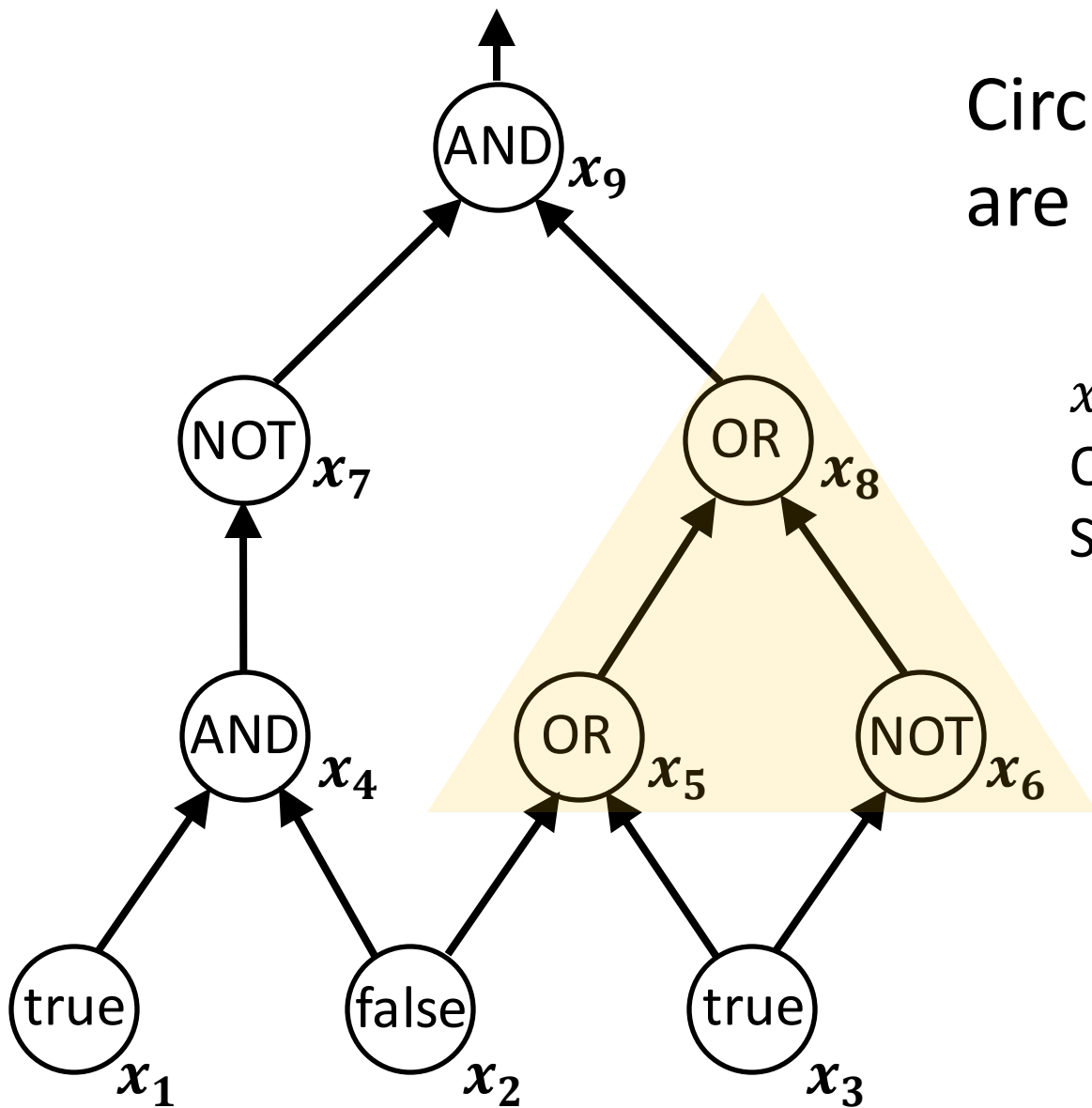Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$


$$x_5 \leq x_2 + x_3$$

$$x_8 \geq x_5$$

$$x_8 \geq x_6$$

$$x_8 \leq x_5 + x_6$$

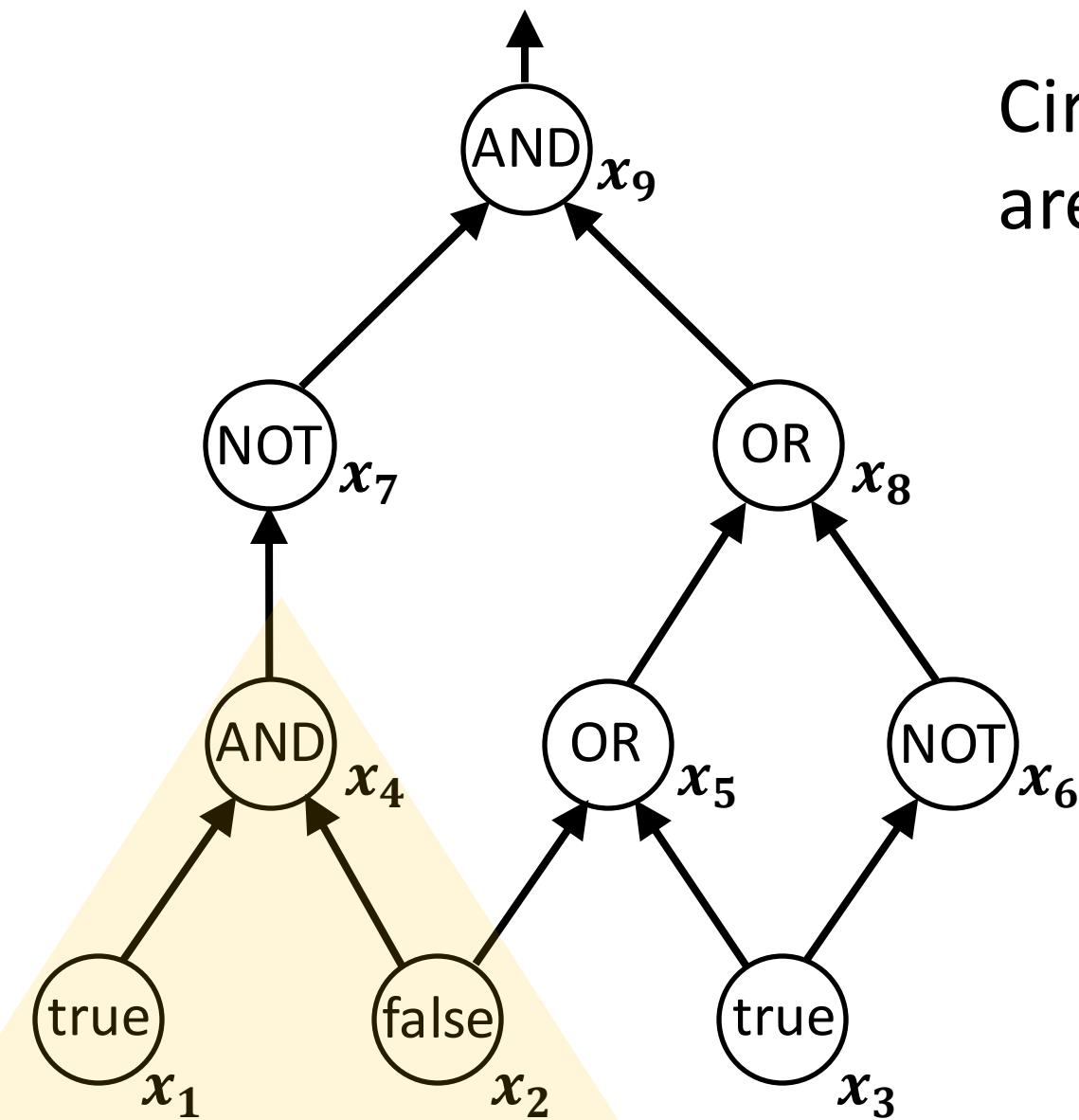Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

$$x_5 \leq x_2 + x_3$$


$$x_8 \geq x_5$$

$$x_8 \geq x_6$$

$$x_8 \leq x_5 + x_6$$

??

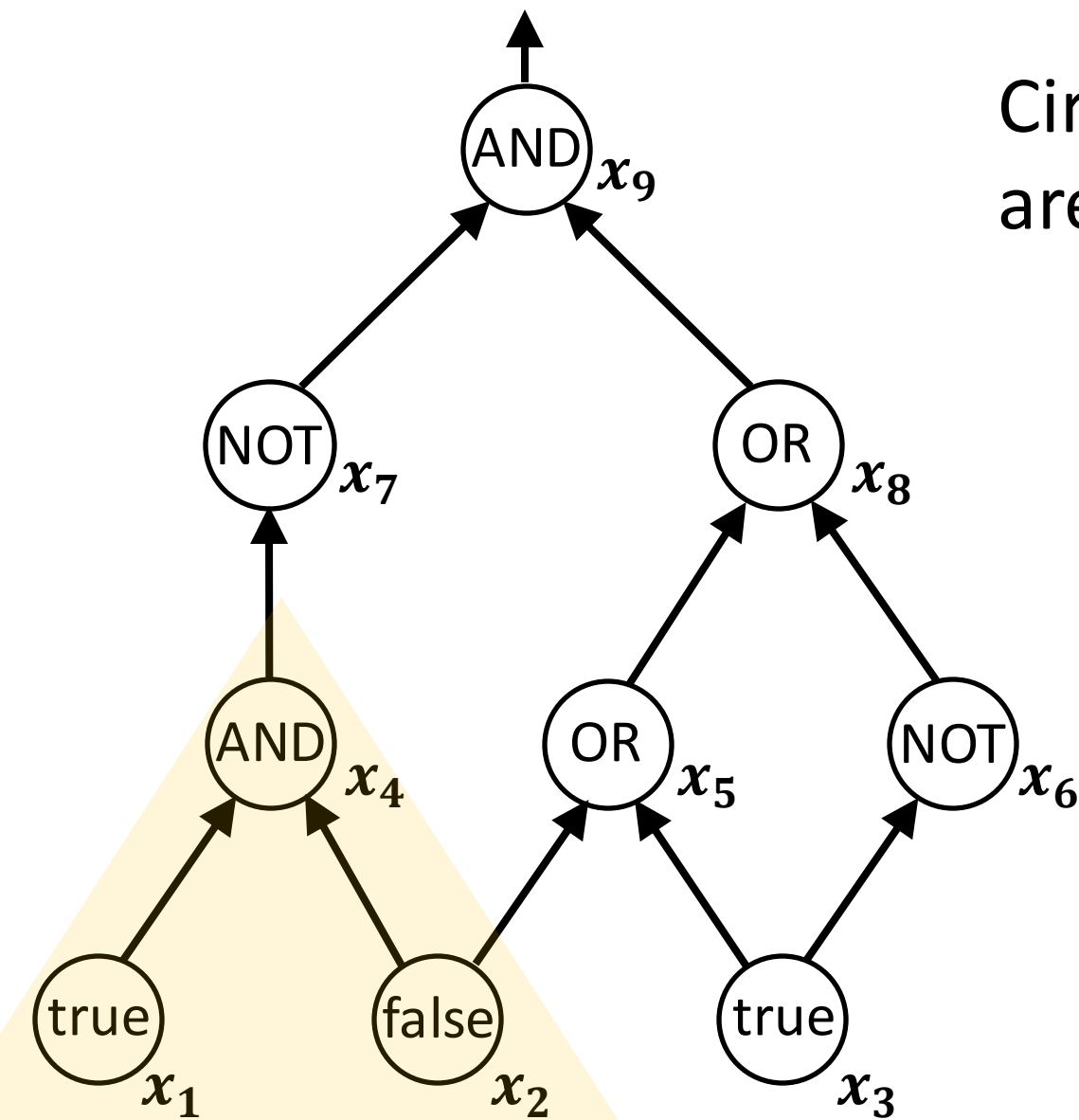Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

$$x_5 \leq x_2 + x_3$$


$$x_8 \geq x_5$$

$$x_8 \geq x_6$$

$$x_8 \leq x_5 + x_6$$

$$x_4 \leq x_1$$

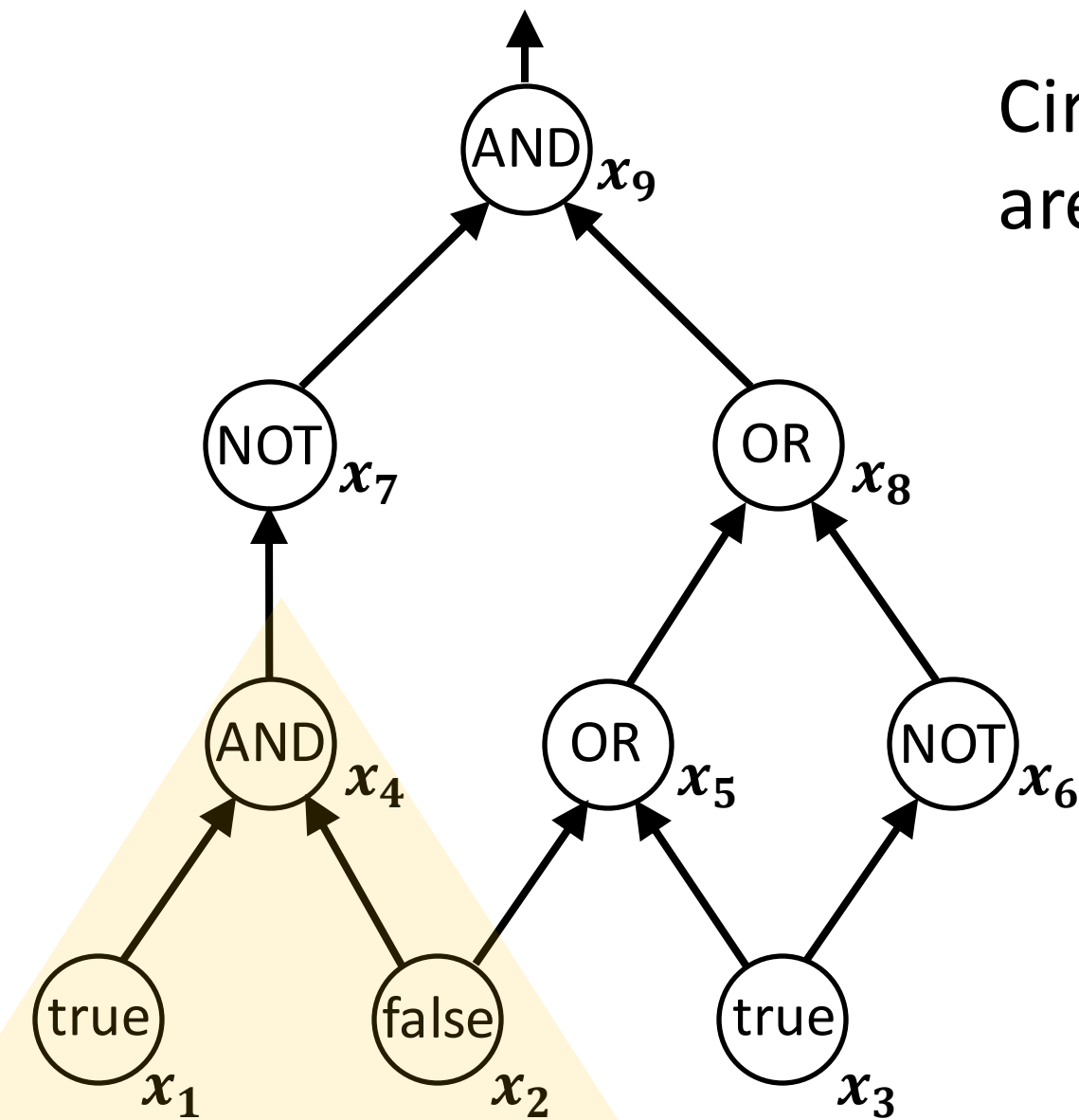Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

$$x_5 \leq x_2 + x_3$$

$$x_8 \geq x_5$$


$$x_8 \geq x_6$$

$$x_8 \leq x_5 + x_6$$

$$x_4 \leq x_1$$

$$x_4 \leq x_2$$

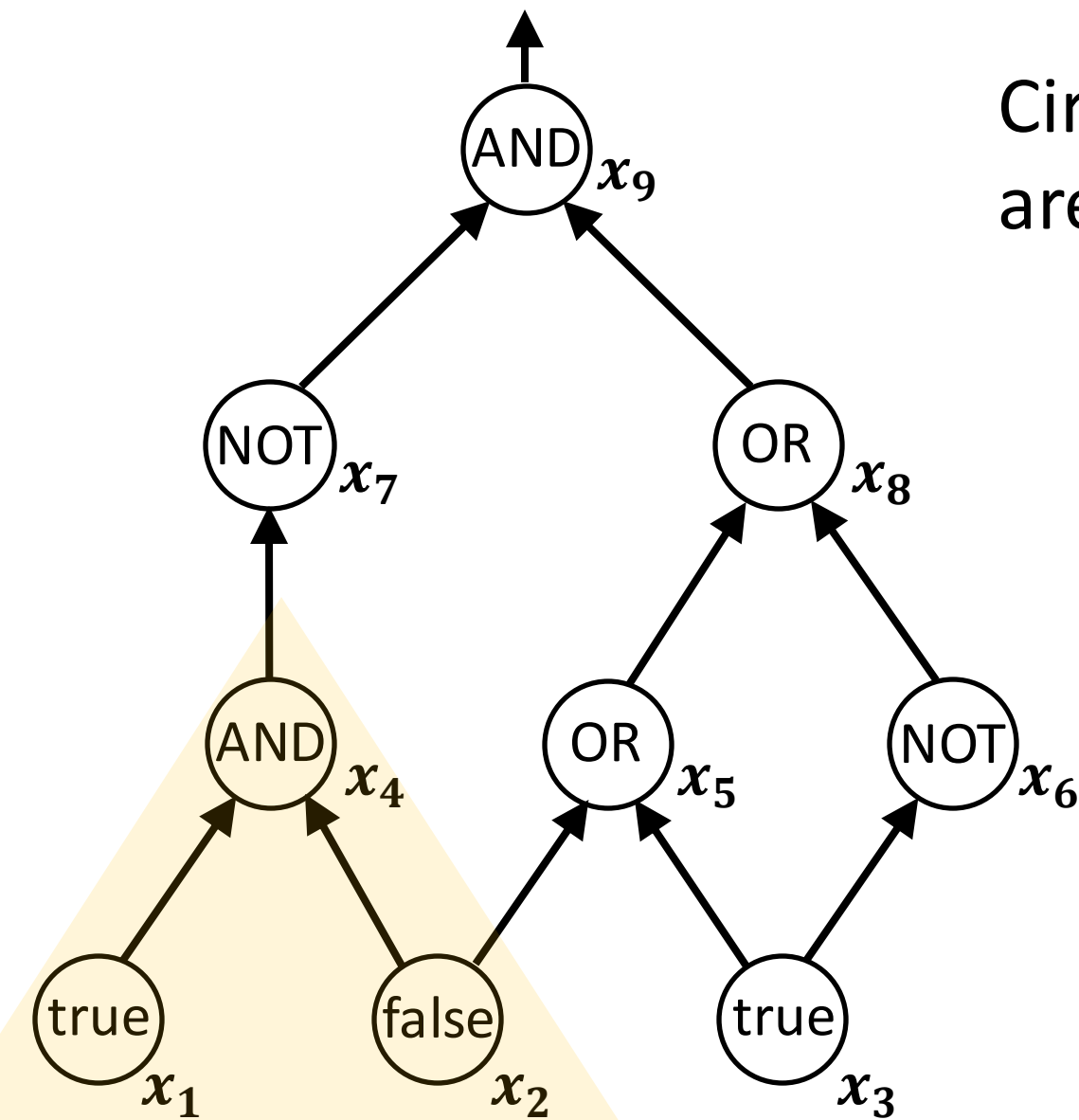Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

$$x_5 \leq x_2 + x_3$$

$$x_8 \geq x_5$$

$$x_8 \geq x_6$$


$$x_8 \leq x_5 + x_6$$

$$x_4 \leq x_1$$

$$x_4 \leq x_2$$

$$x_4 \geq x_1 + x_2 - 1$$

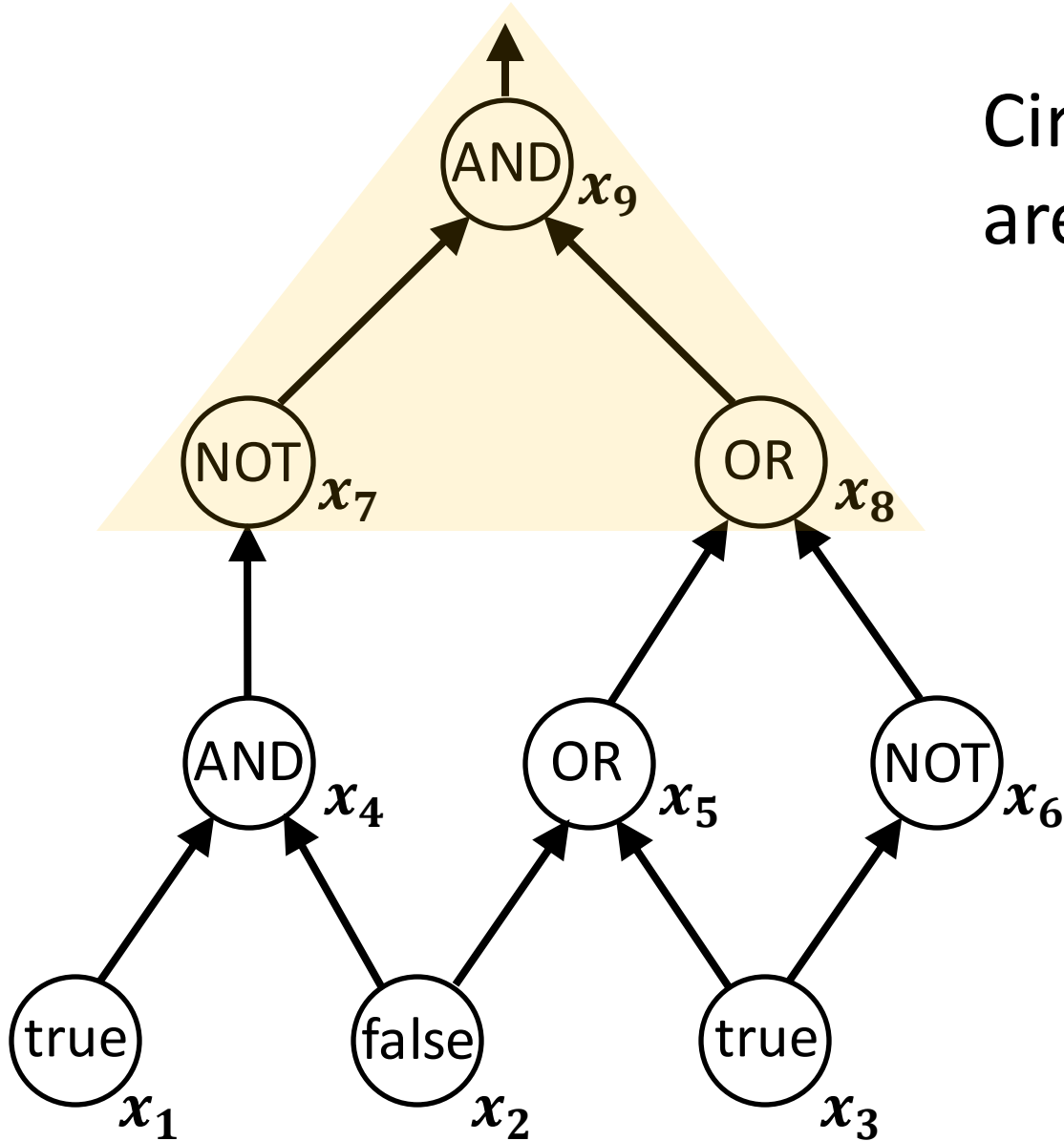Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: ??

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

$$x_5 \leq x_2 + x_3$$

$$x_8 \geq x_5$$

$$x_8 \geq x_6$$

$$x_8 \leq x_5 + x_6$$

$$x_4 \leq x_1$$

$$x_4 \leq x_2$$


$$x_4 \geq x_1 + x_2 - 1$$

$$x_9 \leq x_7$$

$$x_9 \leq x_8$$

$$x_9 \geq x_7 + x_8 - 1$$

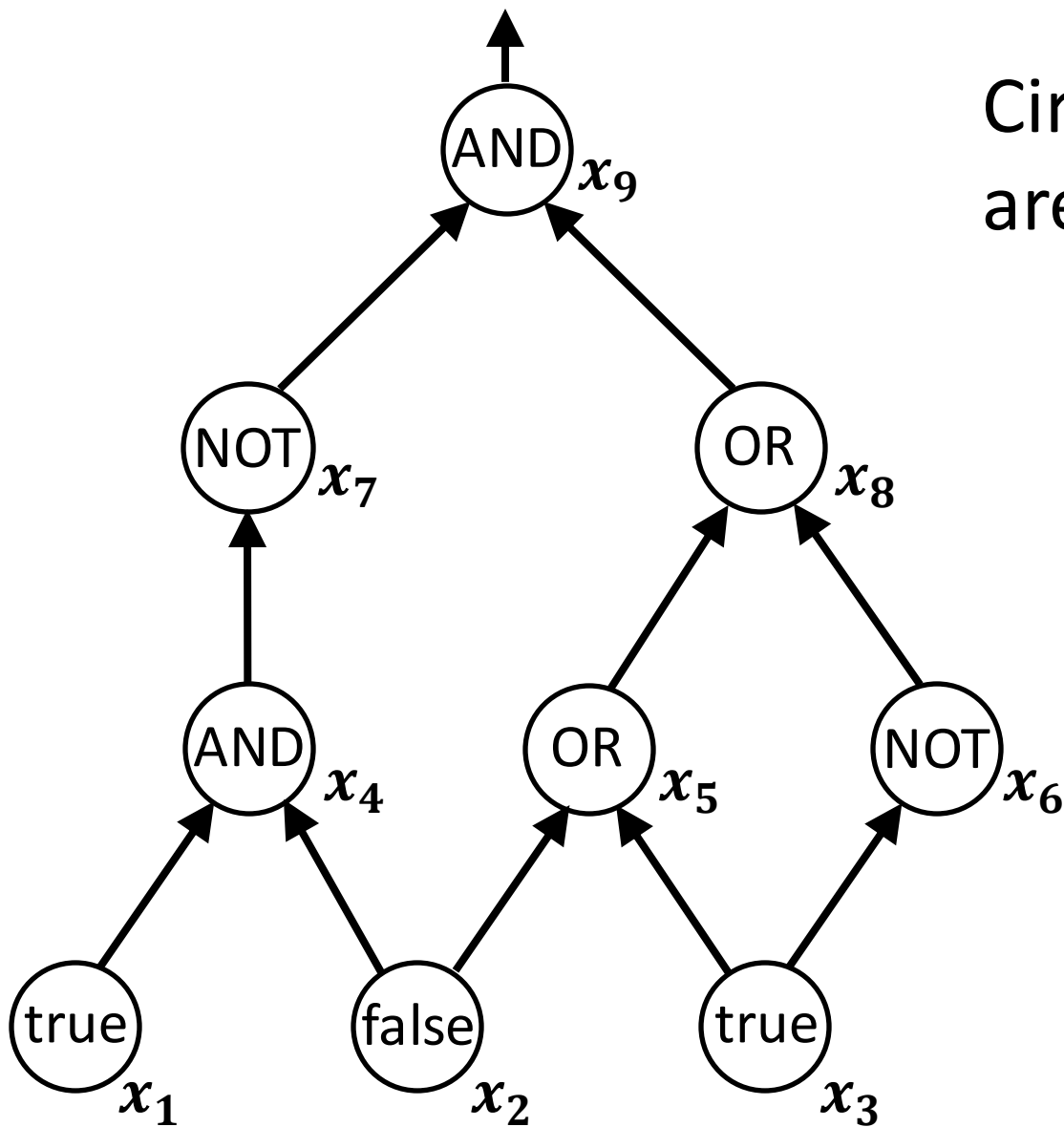Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective:

??

Subject to:

$$x_i \in [0,1], \forall i$$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

$$x_5 \leq x_2 + x_3$$

$$x_8 \geq x_5$$

$$x_8 \geq x_6$$

$$x_8 \leq x_5 + x_6$$

$$x_4 \leq x_1$$

$$x_4 \leq x_2$$


$$x_4 \geq x_1 + x_2 - 1$$

$$x_9 \leq x_7$$

$$x_9 \leq x_8$$

$$x_9 \geq x_7 + x_8 - 1$$

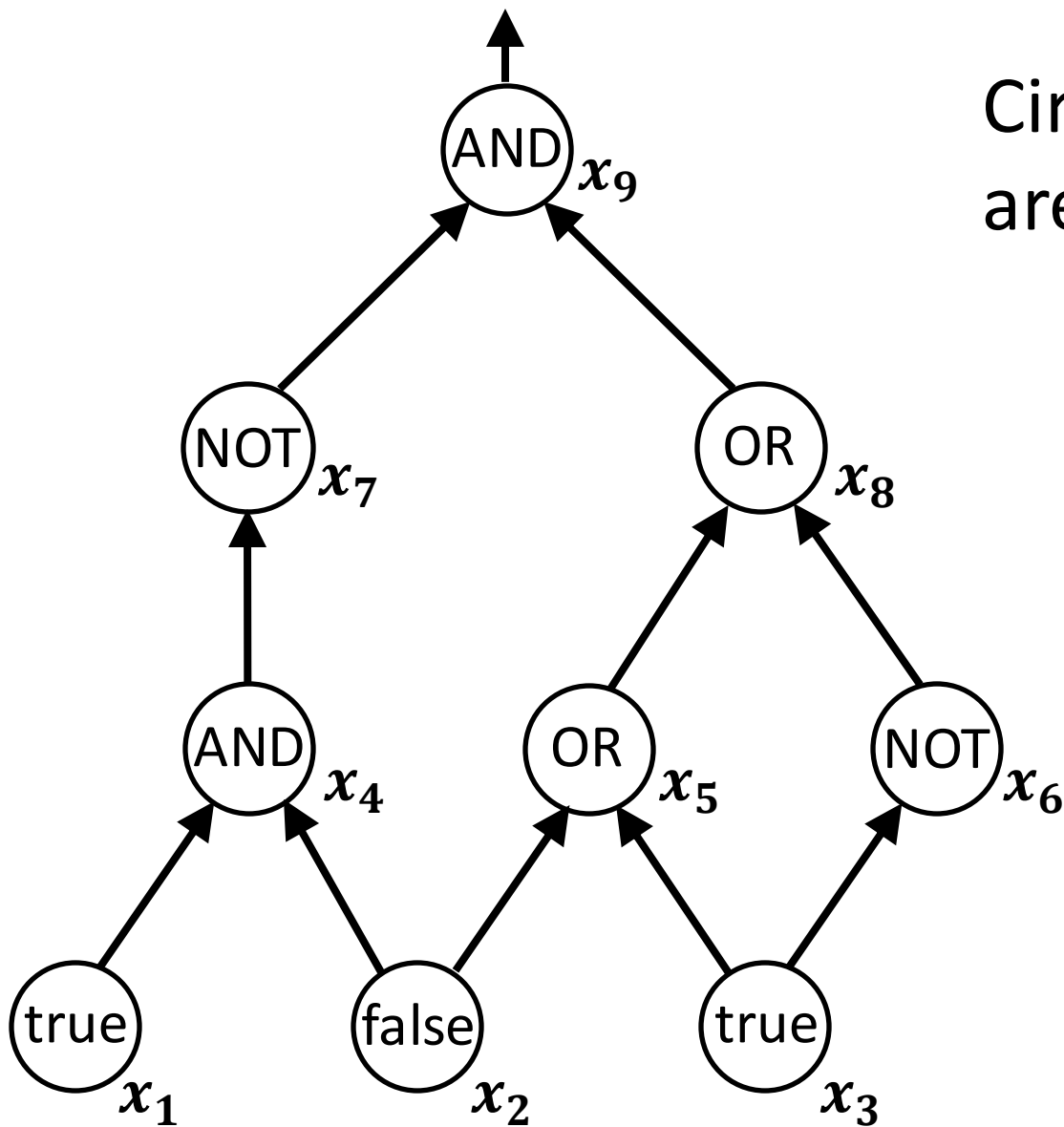Circuit Value Problem: When the gates are evaluated, is the output true?



x_i = gate's evaluated value

Objective: $\min 0$

Subject to: $x_i \in [0,1], \forall i$

$$x_1 = 1$$

$$x_2 = 0$$

$$x_3 = 1$$

$$x_6 = 1 - x_3$$

$$x_7 = 1 - x_4$$

$$x_5 \geq x_2$$

$$x_5 \geq x_3$$

$$x_5 \leq x_2 + x_3$$

$$x_8 \geq x_5$$

$$x_8 \geq x_6$$

$$x_8 \leq x_5 + x_6$$

$$x_4 \leq x_1$$


$$x_4 \leq x_2$$

$$x_4 \geq x_1 + x_2 - 1$$

$$x_9 \leq x_7$$

$$x_9 \leq x_8$$

$$x_9 \geq x_7 + x_8 - 1$$

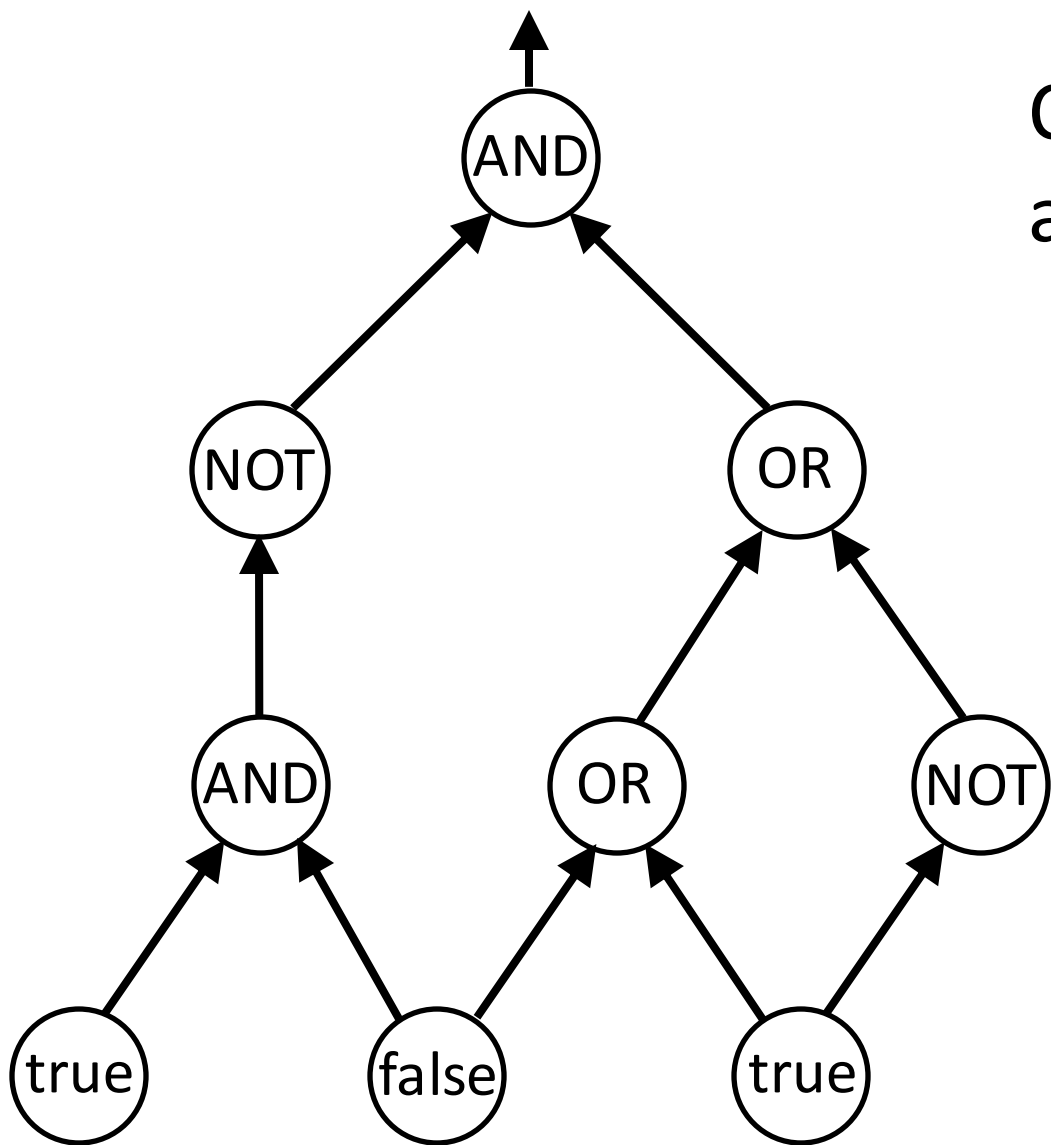


Circuit Value Problem: When the gates are evaluated, is the output true?


x_i = gate's evaluated value

Objective: $\min 0$


Subject to: $x_i \in [0,1]$

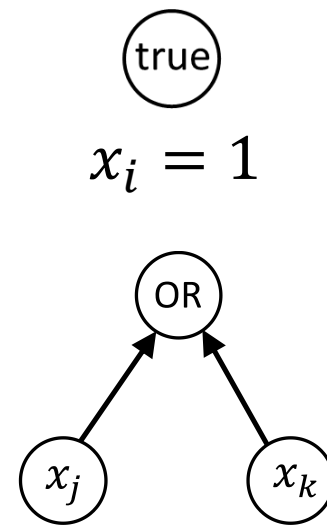

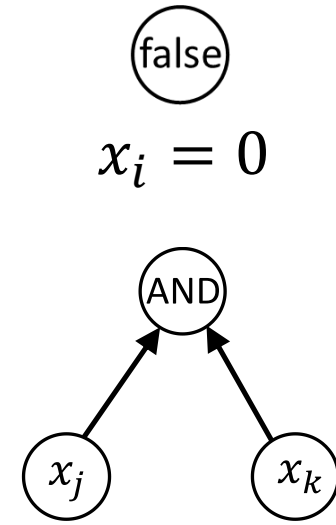
$$\begin{aligned} x_i &\geq x_j \\ x_i &\geq x_k \\ x_i &\leq x_j + x_k \end{aligned}$$


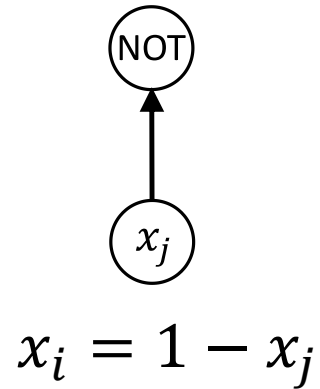
$$\begin{aligned} x_i &\leq x_j \\ x_i &\leq x_k \\ x_i &\geq x_j + x_k - 1 \end{aligned}$$



$$x_i = 1 - x_j$$

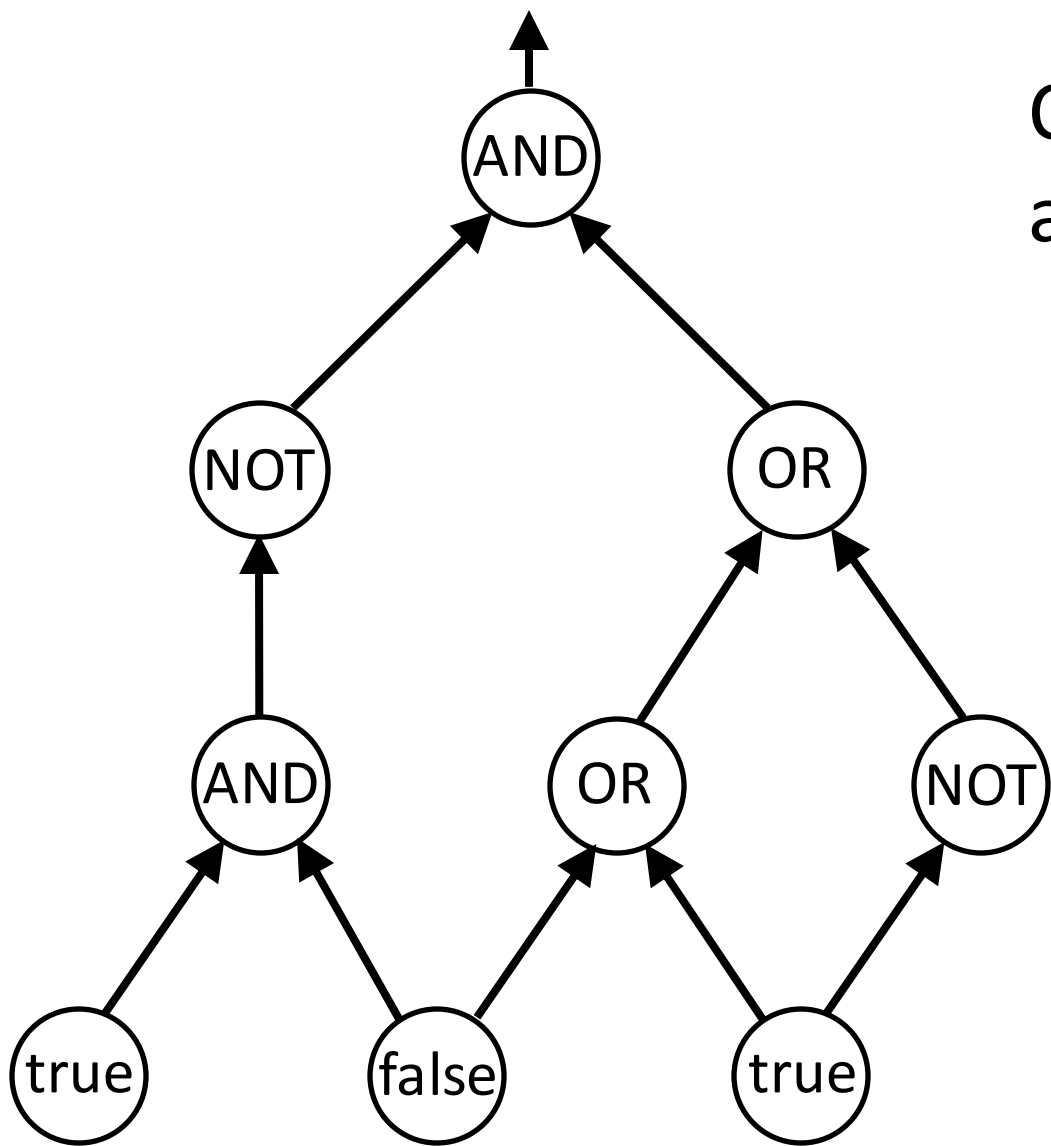


Circuit Value Problem: When the gates are evaluated, is the output true?

x_i = gate's evaluated value


Objective: $\min 0$

Subject to: $x_i \in [0,1]$


Will answer be an integer?

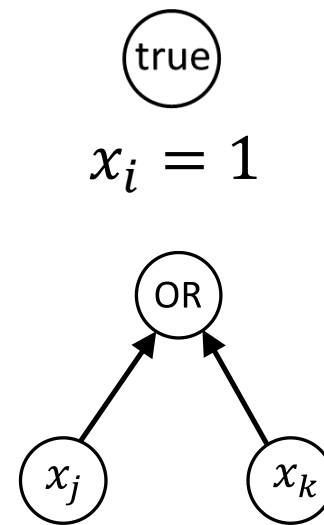

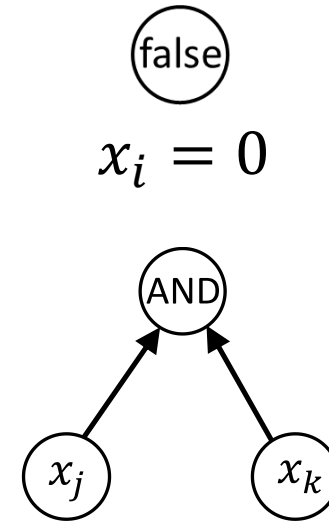
$$\begin{aligned} x_i &\geq x_j \\ x_i &\geq x_k \\ x_i &\leq x_j + x_k \end{aligned}$$


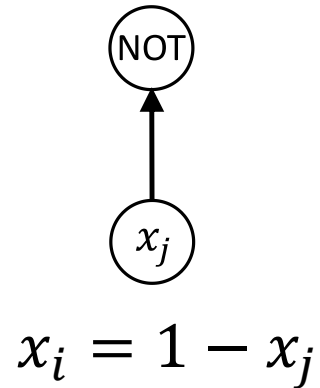
$$\begin{aligned} x_i &\leq x_j \\ x_i &\leq x_k \\ x_i &\geq x_j + x_k - 1 \end{aligned}$$



$$x_i = 1 - x_j$$

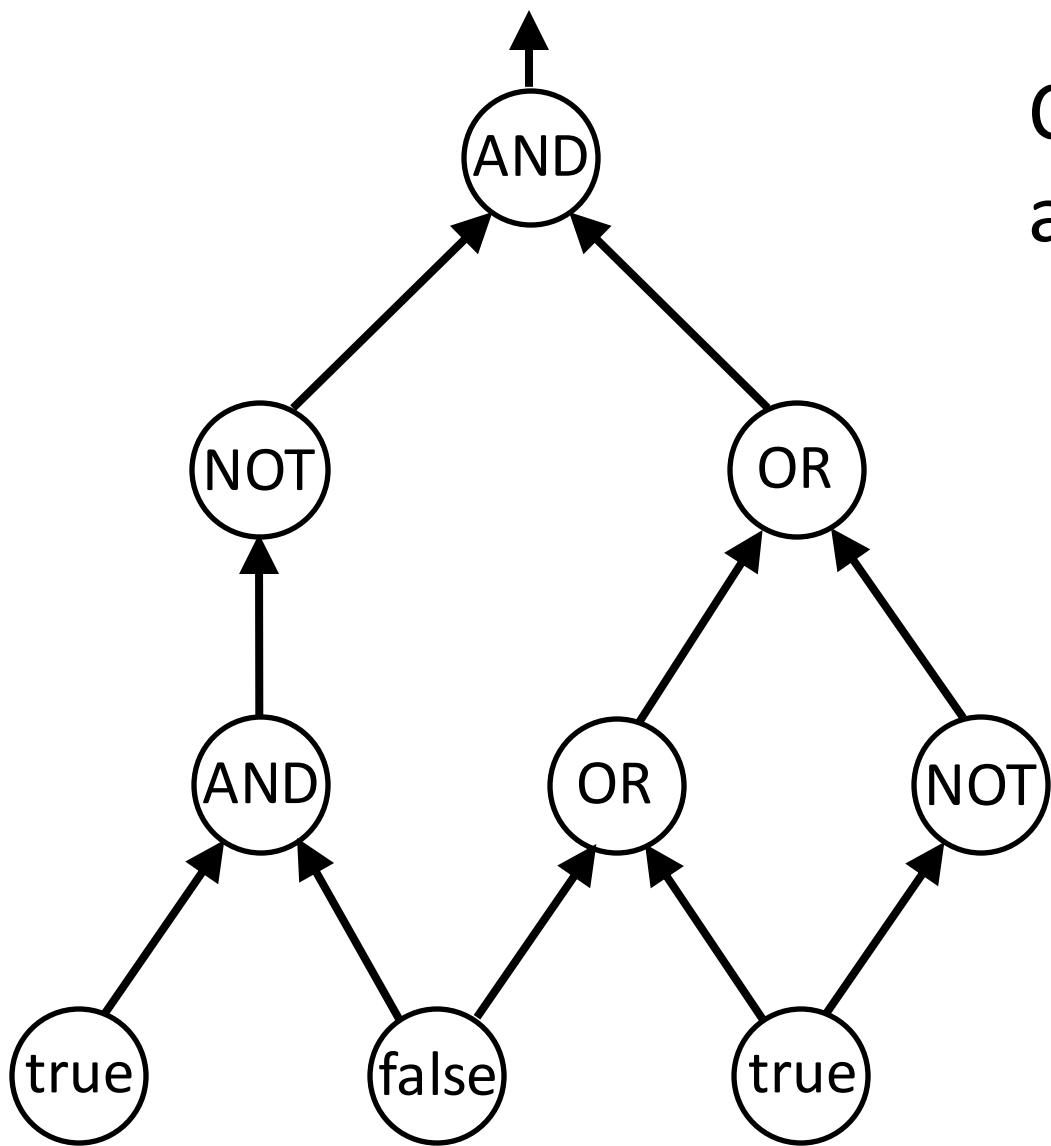

Circuit Value Problem: When the gates are evaluated, is the output true?


x_i = gate's evaluated value

Objective: $\min 0$

Subject to: $x_i \in [0,1]$

Will answer be an integer?

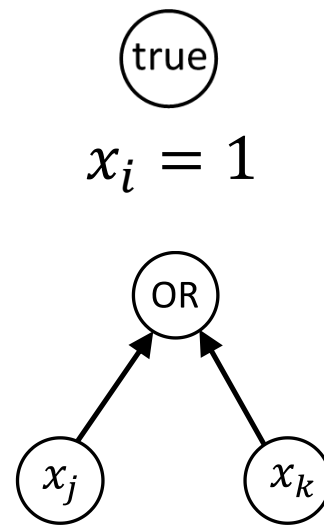
Yes! Input are integers and constraints keep them integers.



$$x_i \geq x_j$$

$$x_i \geq x_k$$


$$x_i \leq x_j + x_k$$

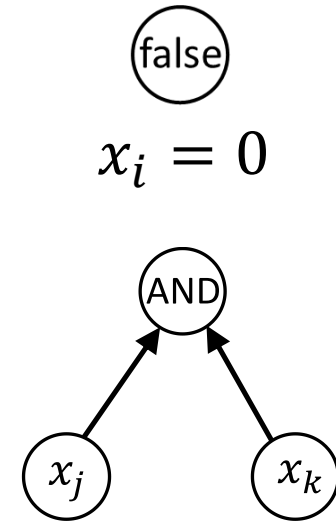


$$x_i \leq x_j$$

$$x_i \leq x_k$$

$$x_i \geq x_j + x_k - 1$$

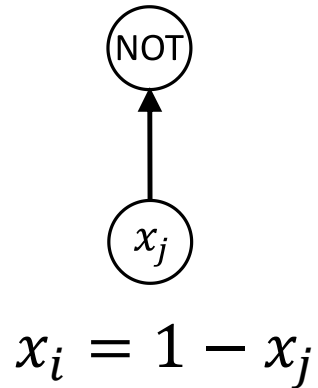

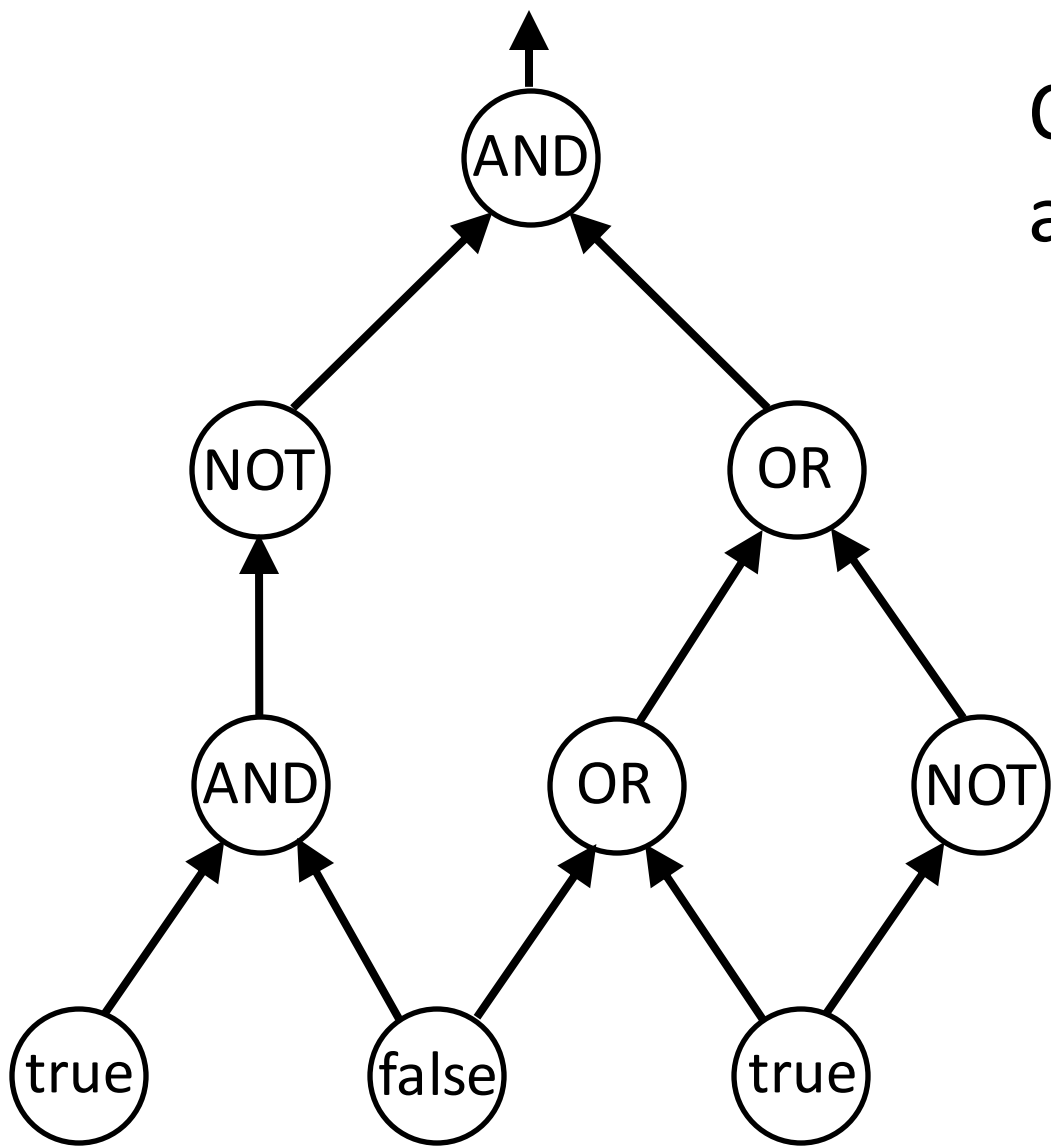


Anything that can run on a computer in poly time can be solved with an LP in poly time!

Circuit Value Problem: When the gates are evaluated, is the output true?

x_i = gate's evaluated value

Objective: $\min 0$

Subject to: $x_i \in [0,1]$

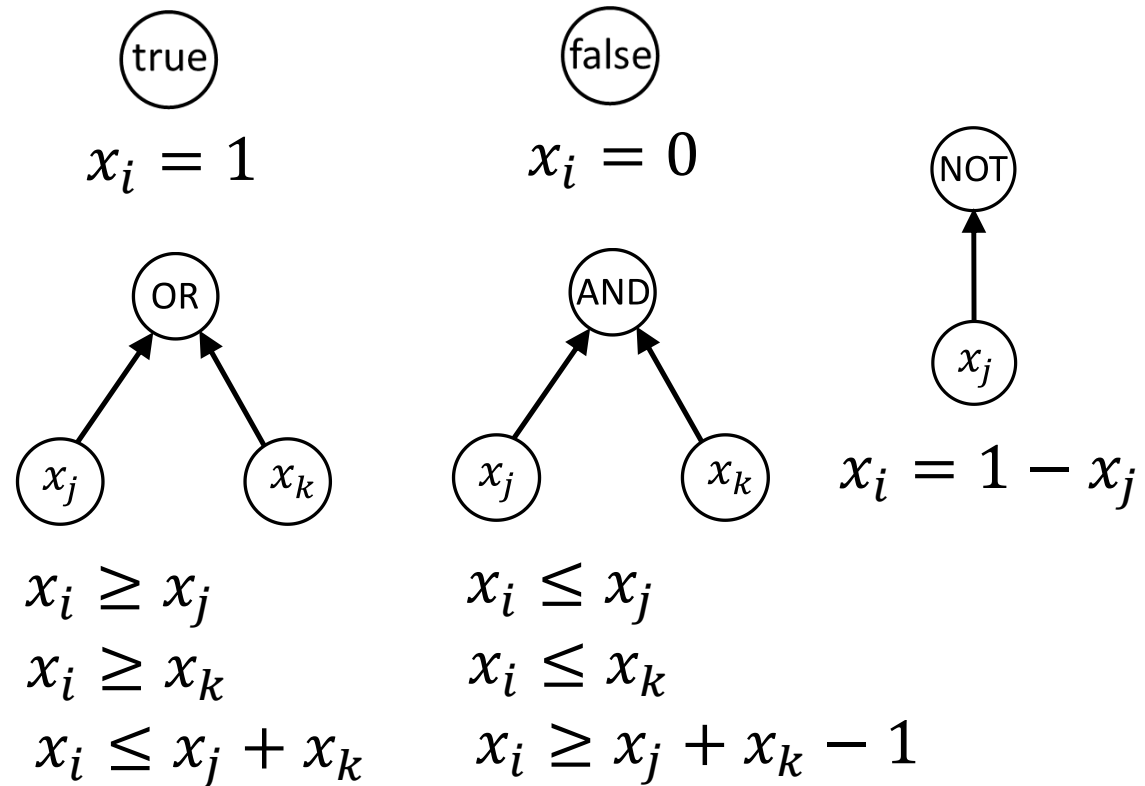

Dual

Primal

Objective: $\max c^T x$

Subject to: $A x \leq b$

$x \geq 0$

Objective: $\max 100x_1 + 300x_2 + 150x_3$

Subject to: $x_2 \leq 20$ A

$x_1 + x_2 + x_3 \leq 40$ B

$2x_1 + x_3 \leq 60$ C

Dual

Objective: $\min b^T y$

Subject to: $A^T y \geq c$

$y \geq 0$

Objective: $\min 20y_1 + 40y_2 + 60y_3$

Subject to: $y_2 + 2y_3 \geq 100$

$y_1 + y_2 \geq 300$

$y_2 + y_3 \geq 150$

$y_1, y_2, y_3 \geq 0$

Dual

Primal

Objective: $\max c^T x$
Subject to: $A x \leq b$
 $x \geq 0$

Dual

Objective: $\min b^T y$
Subject to: $A^T y \geq c$
 $y \geq 0$

Theorem: The dual of a dual is the original primal.

Theorem: If \bar{x} is any feasible solution to the primal and \bar{y} is any feasible solution to the dual, then $c^T \bar{x} \leq b^T \bar{y}$.

Theorem: If \bar{x} is the optimal solution to the primal and \bar{y} is the optimal solution to the dual, then $c^T \bar{x} = b^T \bar{y}$.

Dual

Primal

Objective: $\max c^T x$
Subject to: $A x \leq b$
 $x \geq 0$

Dual

Objective: $\min b^T y$
Subject to: $A^T y \geq c$
 $y \geq 0$

Maximum Flow

???

Theorem: The dual of a dual is the original primal.

Theorem: If \bar{x} is any feasible solution to the primal and \bar{y} is any feasible solution to the dual, then $c^T \bar{x} \leq b^T \bar{y}$.

Theorem: If \bar{x} is the optimal solution to the primal and \bar{y} is the optimal solution to the dual, then $c^T \bar{x} = b^T \bar{y}$.

Dual

Primal

Objective: $\max c^T x$
Subject to: $A x \leq b$
 $x \geq 0$

Maximum Flow

Dual

Objective: $\min b^T y$
Subject to: $A^T y \geq c$
 $y \geq 0$

Minimum Cut

Theorem: The dual of a dual is the original primal.

Theorem: If \bar{x} is any feasible solution to the primal and \bar{y} is any feasible solution to the dual, then $c^T \bar{x} \leq b^T \bar{y}$.

Theorem: If \bar{x} is the optimal solution to the primal and \bar{y} is the optimal solution to the dual, then $c^T \bar{x} = b^T \bar{y}$.